



JOINT INSTITUTE  
交大密西根学院

# ECE3110J/VE311 Electronic Circuits



## Mid-term Summary

Yuljae Cho, *PhD*  
Associate Professor  
Joint Institute, SJTU




 
 
# PN Junction Diode

The **pn junction diode** is formed by fabrication of a p-type semiconductor region in intimate contact with an n-type semiconductor region.




Non-linear, or rectifying, behavior

# PN diode Physics

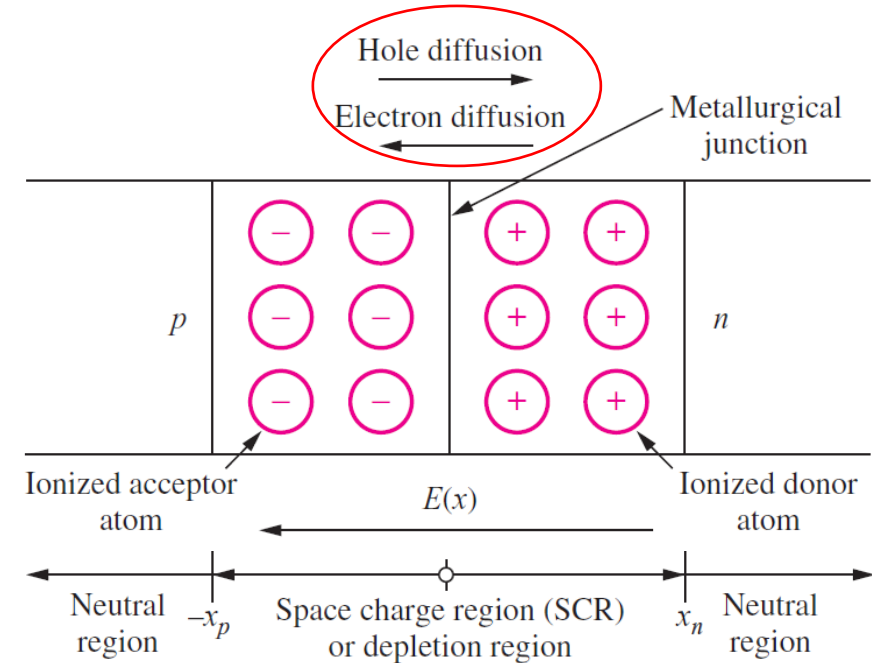  


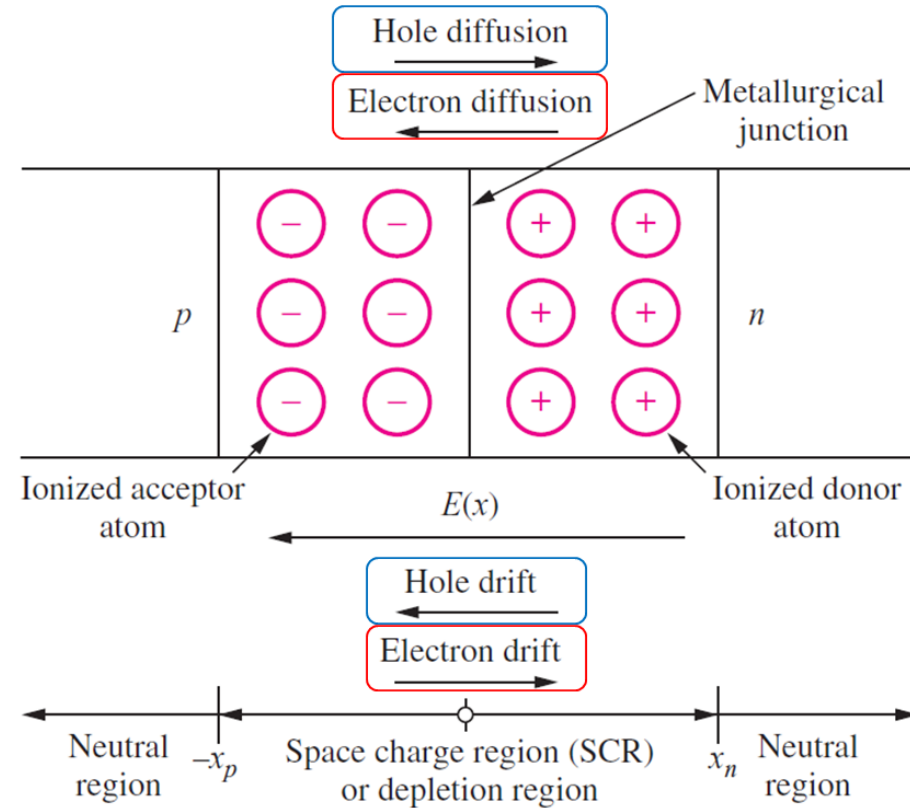As a result of the diffusion of charges, immobile ionized charges (atoms) are revealed, generating an electric field, or **built-in potential**.





The carriers **drift in directions opposite the diffusion** of the same carrier species. Because the terminal currents must be zero, a **dynamic equilibrium** is established in the junction region. Hole diffusion is precisely balanced by hole drift, and electron diffusion is exactly balanced by electron drift.

# I-V Characteristics of Diode

 

**Under Bias (Non Equilibrium)**

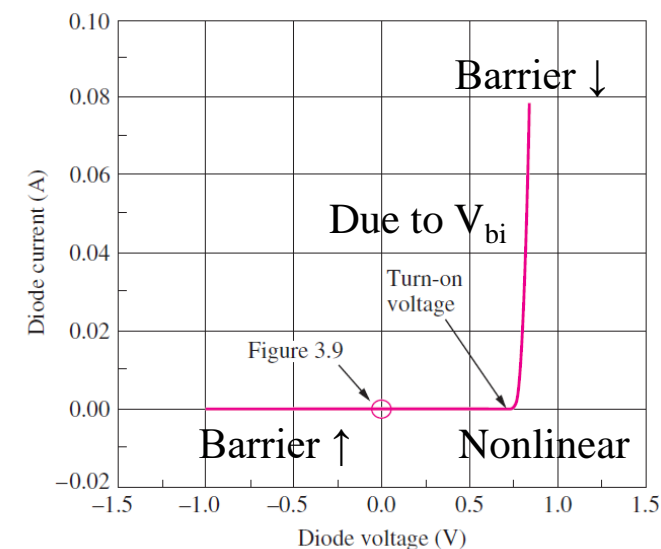 




The diode permits **current to flow in one direction in a circuit**, but prevents movement of current in the opposite direction **due to the barrier, or built-in potential**. We will find that this nonlinear behavior has many useful applications in electronic circuit design.

- Turn-on voltage typically 0.5 to 0.7 V
- Saturation current ( $I_S$ ) typically  $10^{-18}$  to  $10^{-9}$  A
- $kT/q = 0.025875$  V at 300 K
 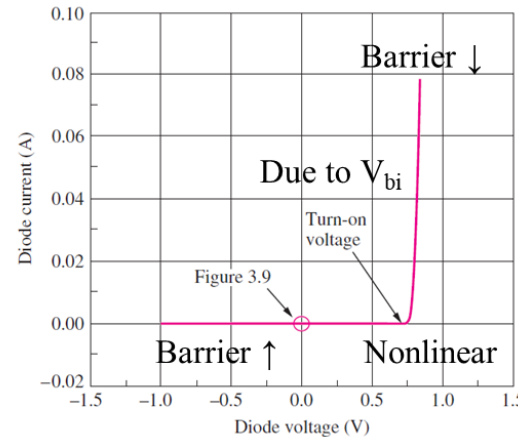 
## Diode Equation and Diode Under Bias

**Forward bias**, i.e.  $v_D > 0$ , **diode is on**: Current flows from P to N

**Reverse bias**, i.e.  $v_D < 0$ , **diode is off**: Current does not flow, but saturation current exists



The total current through the diode is  $i_D$ , and the voltage drop across the diode terminals is  $v_D$ .


$I_D = I_S \left( e^{\frac{qV_d}{kT}} - 1 \right)$  **or**  $I_S (e^{v_D/v_T} - 1)$  where  $k$  is Boltzmann's constant.

e.g.  $v_D = 1 \text{ V}$ ,  $i_D = I_S (e^{v_D/v_T} - 1) = I_S (e^{1/0.025} - 1)$

e.g.  $v_D = -1 \text{ V}$ ,  $i_D = I_S (e^{v_D/v_T} - 1) = I_S (e^{-1/0.025} - 1) = I_S * (-1) \approx -I_S$
 
## Diode Circuit Analysis

One common objective of diode circuit analysis is to find the **quiescent operating point** (Q-point), or **bias point**, for the diode. The Q-point consists of the dc current and voltage ( $I_D$ ,  $V_D$ ) that define the point of operation on the diode's  $i$ - $v$  characteristic.




$$V = I_D R + V_D$$

$$I_D = ?$$

$$V_D = ?$$

- ~~1.~~ Graphical analysis
- ~~2.~~ Mathematical analysis
3. Simplified analysis (ideal diode)
4. Simplified analysis (constant voltage drop)


## Simplified Analysis (Ideal Diode)

 

Though the diode  $i$ - $v$  curve is not linear we can use **piecewise linear** approximations for the diode  $i$ - $v$  characterization. The **ideal diode model** is the simplest model for the diode. The  $i$ - $v$  characteristic for the **ideal diode consists of two straight-line segments**.



## (1) Forward bias

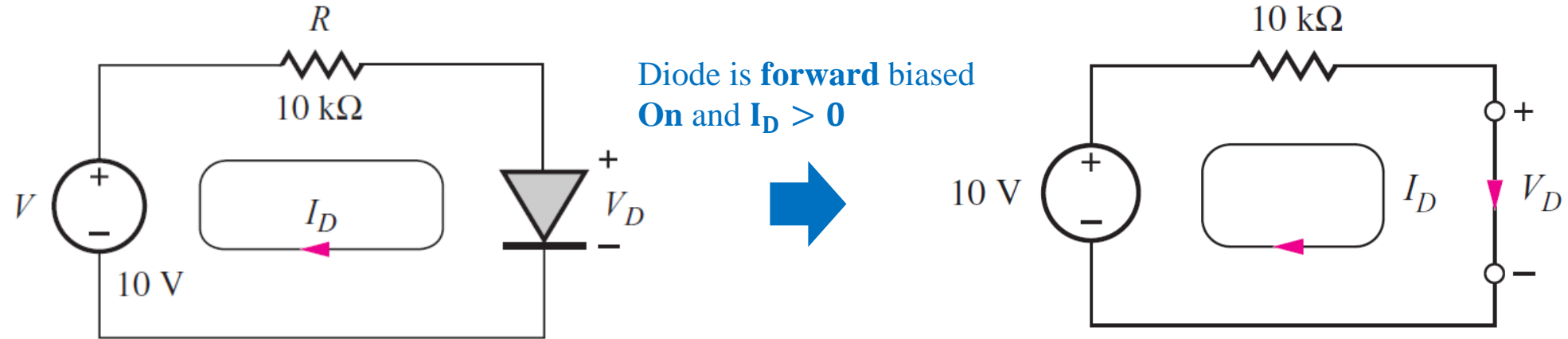


Based on the ideal diode model, we can find that the diode is forward biased and operating with a current of 1 mA as follows.

$$I_D = \frac{10\text{ V}}{10\text{ k}\Omega} = 1\text{ mA}$$

Q-point is 0 V and 1 mA.

## (2) Reverse bias


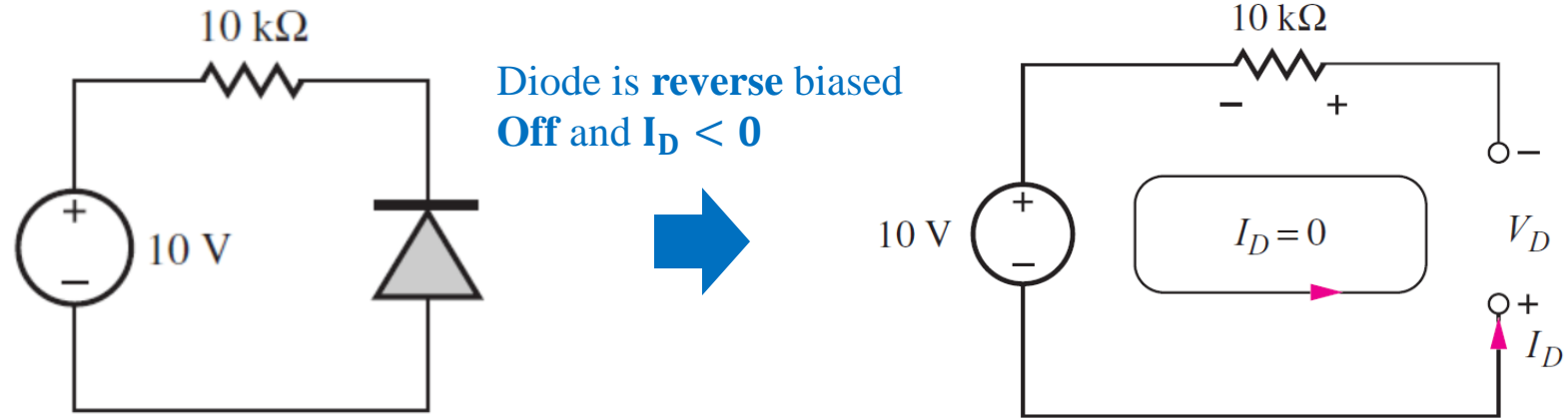


As the diode is off, the circuit is open.

$I_D = 0$  and  $V_D = -10$  V



Q-point is -10 V and 0 A.
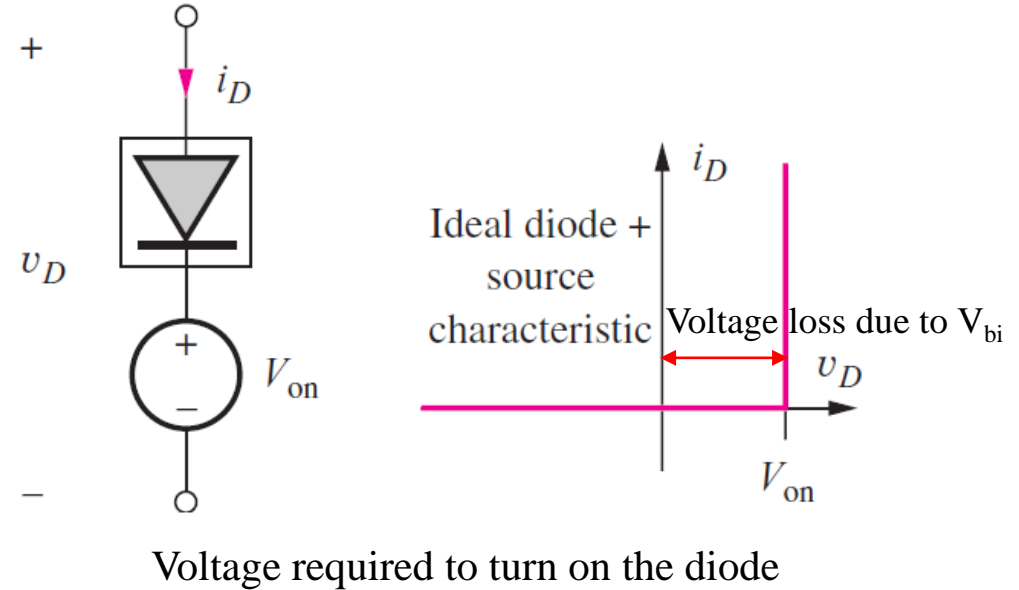 
## Simplified Analysis (Constant Voltage Drop)



The diode current flows when electric charges **overcome the built-in potential**, i.e. voltage loss, which can be viewed as the **turn-on voltage  $V_{on}$**  of the diode. The piecewise linear model for the diode can be improved by adding a constant voltage  $V_{on}$  in series with the ideal diode. This is the **constant voltage drop (CVD) model**.

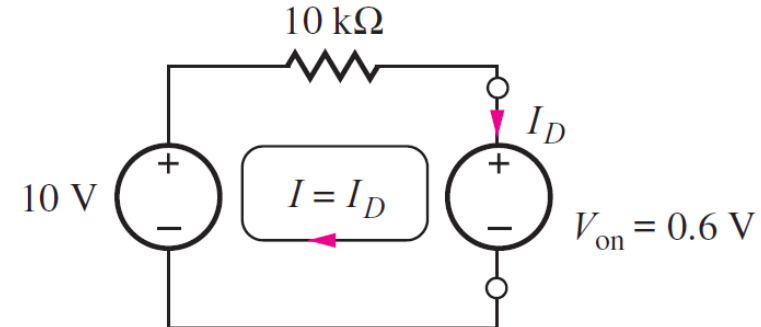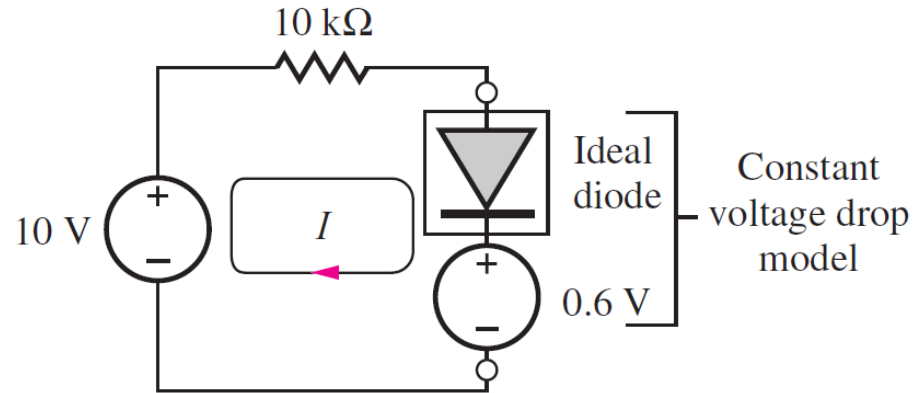We can think  $V_{on}$  as the voltage required to turn on the diode by overcoming  $V_{bi}$ .



The diode is forward biased and thus the diode is on with 0.6 V of voltage loss in the circuit.

$$V_D = V_{on} = \mathbf{0.6 \text{ V}} \text{ and } I_D = \frac{10 - 0.6}{10k\Omega} = \mathbf{0.94 \text{ mA}}$$

Thus, Q-point is 0.6 V and 0.94 mA.


## Half-Wave Rectifier Circuit

**The basic rectifier circuit converts an ac voltage to a pulsating dc voltage.** A filter is added to eliminate the ac components of the waveform and produce a nearly constant dc voltage output. In fact, majority of electronic circuits are powered by a dc source, usually based on some form of rectifier.



<b>Input Voltage</b>	<b>240 Volts (AC)</b>
<b>Wattage</b>	65 watts
<b>Output Voltage</b>	<b>19.5 Volts (DC)</b>
<b>Power Source</b>	Corded Electric
<b>Current Rating</b>	3.34 Amps
<b>Frequency Range</b>	60 hertz



 
Frequency: 50 to 60 Hz, single phase  
Line Voltage: **100 to 240 VAC**  
Output Voltage/Current: **9 VDC/2.2 A**  
Minimum Power Output: 20 W





# Half-wave rectifier with resistor load

 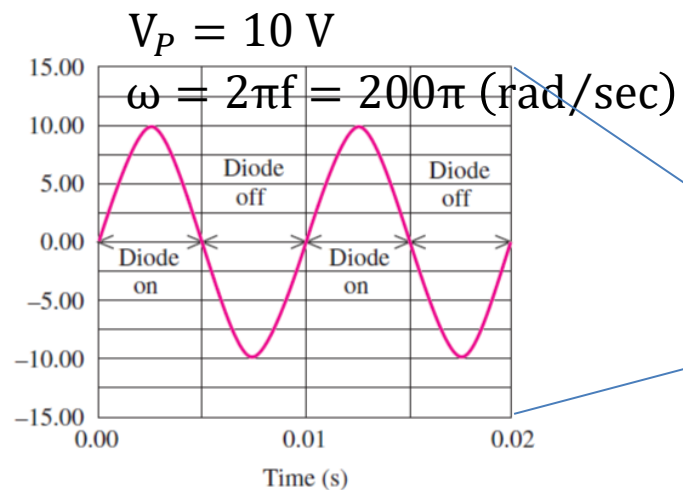

$V_I > 0$ ,  $D_1$  is on

 


$V_I < 0$ ,  $D_1$  is off

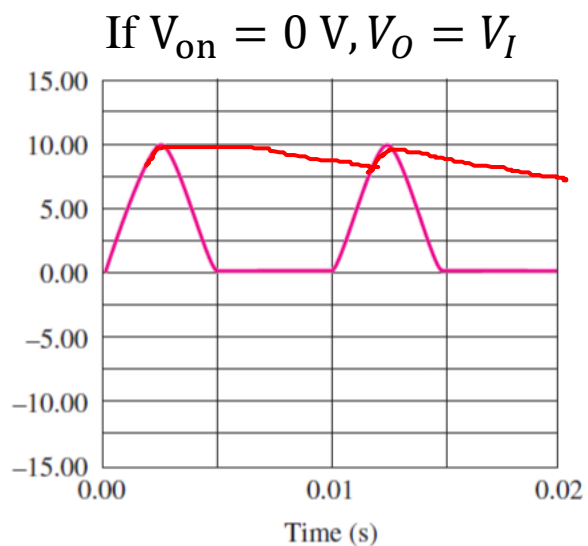 

DC like.  
 $v_o$  is not DC.

 
If  $V_{on} = 0.7\text{ V}$ ,  $V_O = V_P \sin \omega t - V_{on}$




$v_o$  is not DC.
 
## Half-Wave Rectifier with RC Load



To understand operation of the rectifier filter, we first consider operation of the peak-detector circuit consisting of the input source, diode, and capacitor. The cap was initially discharged  $V_o(0) = 0 \text{ V}$



 No path for cap discharge when diode is off



  By connecting a load  $R$  to the peak-detector circuit, now we provide power to the load  $R$ , meaning that **there is a path available to discharge the capacitor** during the time the diode is not conducting.




The output voltage is no longer constant, but has a **ripple voltage  $V_r$** . Also, the **diode only conducts for a short time  $\Delta T$**  during each cycle. We are interested in three parameters:

- (1) Ripple voltage  $V_r$
- (2) Conduction interval  $\Delta T$
- (3) Conduction angle  $\theta_c = \omega \Delta T$



# Ripple Voltage

 

$\Delta T$ : Diode ON

Recall VE215, a **RC response** without a source (discharge period) is

$$v_o(t) = (V_P - V_{on}) \exp\left(-\frac{t}{RC}\right)$$

Ripple voltage  $V_r$  can be described as

$V_r = \text{Peak point} - \text{RC response}$

$$= (V_P - V_{on}) - v_o(t)$$

$$= (V_P - V_{on}) \left[ 1 - \exp\left(-\frac{T - \Delta T}{RC}\right) \right]$$

When diode is off, i.e.  
RC response

Discharging period


By Taylor series,  $e^{-x} = 1 - x$ , **ripple voltage**  $V_r$  becomes

$$V_r = (V_P - V_{on}) \left[ 1 - \left( 1 - \frac{T - \Delta T}{RC} \right) \right], \text{ and to attain stable DC } V_r \text{ needs to be minimized.}$$

From the graph above, we can see that if  $\Delta T \ll T$ ,  $V_r$  becomes smaller.

$$\text{Thus, finally, } V_r = \frac{(V_P - V_{on}) T}{R C}$$

## Conduction angle and interval

 

At  $5/4T - \Delta T$ , the input voltage ( $V_P - V_{on}$ ) just exceeds the output voltage ( $V_O$ ). **Diode is ON.**

$$\Theta = \omega t = 2\pi f \cdot t = \frac{2\pi}{T} \left( \frac{5}{4}T - \Delta T \right) = \frac{5\pi}{2} - \theta_c \text{ as } \theta_c = \omega \Delta T$$

At  $5/4T - \Delta T$ , Input sine wave  $- V_{on} = (\text{Peak of Sine wave} - V_{on}) - V_r$

$$V_P \sin \left[ \omega \left( \frac{5T}{4} - \Delta T \right) \right] - V_{on} = (V_P - V_{on}) - V_r$$



$$\rightarrow V_P \sin \left( \frac{5\pi}{2} - \theta_c \right) - V_{on} = (V_P - V_{on}) - V_r$$

Thus, the equation becomes  $V_P \cos \theta_c = V_P - V_r \rightarrow \cos \theta_c = \frac{V_P - V_r}{V_P} \cong 1 - \frac{\theta_c^2}{2}$  if  $\theta_c$  is very small

$$\theta_c = \sqrt{\frac{2V_r}{V_P}} \quad \Delta T = \frac{\theta_c}{\omega} = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}}$$
  
## Diode Current

Diode current flows for only a very small fraction of the period  $T$ . **The capacitor is charged during  $\Delta T$  and is discharged during  $T - \Delta T$ .**




$$Q \cong \frac{I_{peak} \Delta T}{2} = I_{dc} (T - \Delta T) \cong I_{dc} T$$

$$\text{where } I_{dc} = \frac{V_p - V_{on}}{R}$$

$$\rightarrow I_{peak} = \frac{2I_{dc} T}{\Delta T}$$
 
## Surge Current



At the first cycle, the capacitor is completely discharged (as we assumed), and therefore, there will be a larger current through the diode. During charging period ( $\Delta T$ ), almost all diode current goes to C.



$$I_{surge} = i_d(t) = C \frac{d(V_P \sin \omega t - V_{on})}{dt} = \omega C V_P \cos \omega t$$
 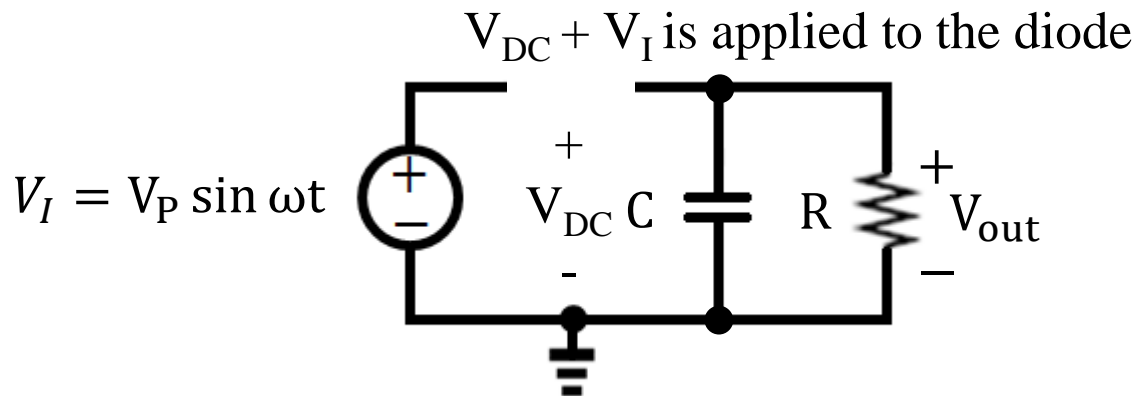
## Peak Inverse Voltage (PIV)



The breakdown voltage rating of the diodes is called the peak-inverse-voltage (VIP). If  $V_r$  is very small, the diode must be able to withstand a large negative peak voltage.



$$\text{Peak-inverse-voltage (PIV)} \geq V_{DC} + V_I = V_P - V_{on} + V_P \cong 2V_P - V_{on}$$

If the diode PIV is smaller than  $2V_P - V_{on}$ , the diode breaks down.

# Full-Wave Bridge Rectifier

  

For  $v_I > 0$ ,  $D_2$  and  $D_4$  will be on and  $D_1$  and  $D_3$  will be off.  
 For  $v_I < 0$ ,  $D_1$  and  $D_3$  will be on and  $D_2$  and  $D_4$  will be off.


$$V_{dc} = V_P - 2V_{on}$$

$$I_{dc} = \frac{V_{dc}}{R}$$

$$V_r = (V_P - 2V_{on}) \left( 1 - e^{-\frac{T/2 - \Delta T}{RC}} \right) \cong (V_P - 2V_{on}) \left( \frac{T/2 - \Delta T}{RC} \right) \text{ if } \left( \frac{T}{2} - \Delta T \right) \ll RC$$

$$\cong (V_P - 2V_{on}) \left( \frac{T}{2RC} \right) \text{ if } \Delta T \ll \frac{T}{2}$$

## Conduction angle and interval

 

$$-V_P \sin \left[ \omega \left( \frac{3T}{4} - \Delta T \right) \right] - 2V_{on} = (V_P - 2V_{on}) - V_r$$


$$-V_P \sin \left( \frac{3\pi}{2} - \theta_c \right) - 2V_{on} = (V_P - 2V_{on}) - V_r$$

$$V_P \cos \theta_c = V_s - V_r$$

$$\cos \theta_c = \frac{V_P - V_r}{V_s} \cong 1 - \frac{\theta_c^2}{2} \text{ if } \theta_c \text{ very small}$$

$$\theta_c = \sqrt{\frac{2V_r}{V_P}}$$
 
$$\Delta T = \frac{\theta_c}{\omega} = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}}$$




$$Q \cong \frac{I_{\text{peak}} \Delta T}{2} = I_{\text{dc}} \left( \frac{T}{2} - \Delta T \right) \cong I_{\text{dc}} \frac{T}{2}$$

$$I_{\text{peak}} = \frac{I_{\text{dc}} T}{\Delta T}$$

$$I_{\text{surge}} = \omega C V_P \text{ (at } t = 0 \text{)}$$


 
$$\text{PIV} = V_P - V_{\text{on}} \cong V_P$$







## Device Schematics

  


BJT has **n<sup>+</sup>-p-n** or **p<sup>+</sup>-n-p** structure.

e.g. n<sup>+</sup>-p-n structure

- Emitter: heavily doped n-type
- Base: p-region
- Collector: lower n-region
- Electron diffusion length ( $L_n$ ) in base  $\gg W_b$
- Emitter doping  $N_{de} \gg$  base doping  $N_{ab}$  ( $I_n \approx I$ )

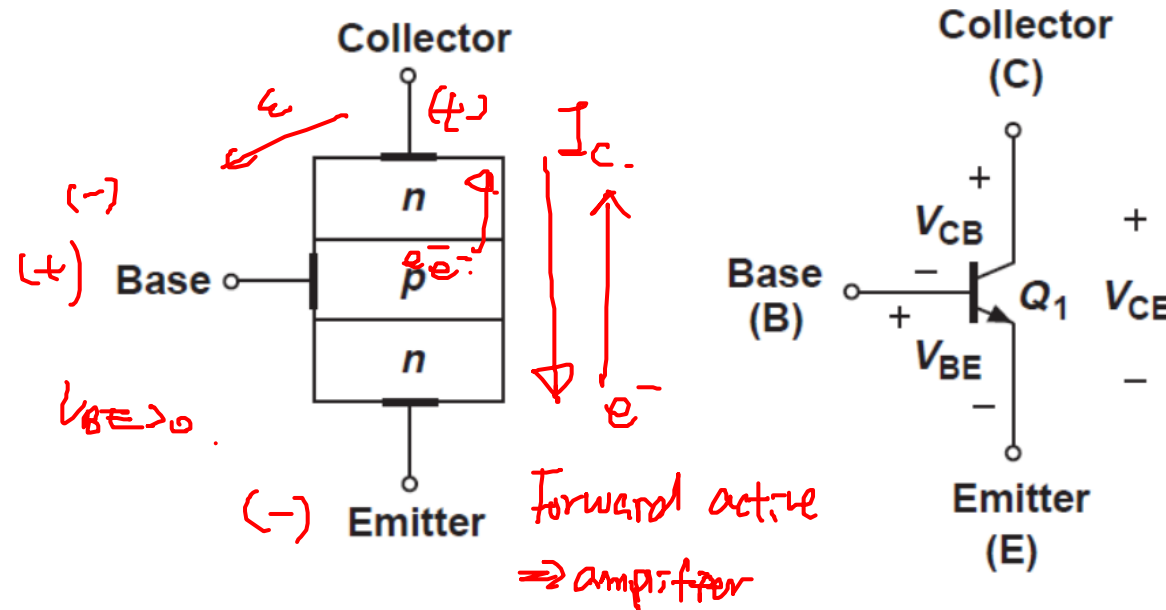
## Structure of BJT

The BJT consists of three doped regions forming a sandwich. Below is an example comprising of a  $p$  layer sandwiched between two  $n$  regions and called an ***n*pn BJT**.



There are three terminal voltages  $V_E$ ,  $V_B$ , and  $V_C$ , and consequently the voltage differences between terminals  $V_{BE}$ ,  $V_{CB}$ , and  $V_{CE}$ . Among various biasing conditions, **for amplification of BJT**, there is **only one biasing condition**.

## Transport Model for NPN BJT


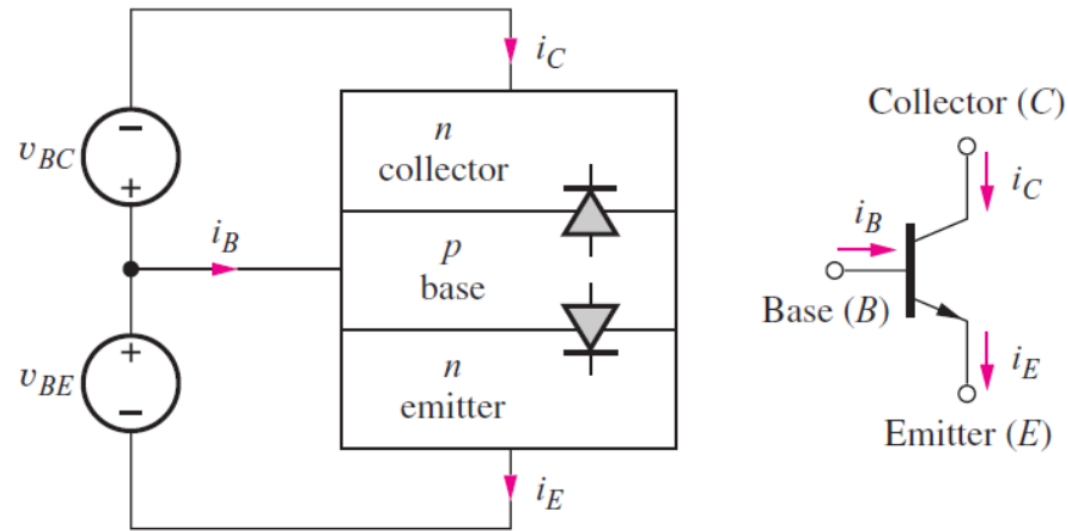


There are also three terminal currents, **collector current  $i_C$** , **emitter current  $i_E$** , and **base current  $i_B$** . The base-emitter voltage  $v_{BE}$  and the base-collector voltage  $v_{BC}$  applied to the two *pn* junctions **determine the magnitude of these three currents in the BJT** and are defined as **positive when they forward-bias** their respective *pn* junctions.

The bias condition for the Forward active mode of BJT (a normal BJT operation mode) is  $v_{BE} > 0$  and  $v_{BC} < 0$ .

### Forward bias

Barrier ↓ and charges flow

  

$V_{CE} \geq V_{BE}$   
 $\Rightarrow$  **Forward – Active**

$V_{BE} > 0$   
 $V_{BC} < 0$



$$i_C = i_F = I_S \left[ e^{v_{BE}/V_T} - 1 \right]$$

$$i_B = i_F / \beta_F = I_S / \beta_F \left[ e^{v_{BE}/V_T} - 1 \right]$$

$$i_E = I_S \left[ e^{v_{BE}/V_T} - 1 \right] + I_S / \beta_F \left[ e^{v_{BE}/V_T} - 1 \right] = \left( I_S + \frac{I_S}{\beta_F} \right) \left[ e^{v_{BE}/V_T} - 1 \right]$$

# Large-Signal Model
  
## IV characteristics – Transfer characteristic





**Transfer characteristic plots  $I_C$  vs  $V_{BE}$**  with the assumption that the  $V_{CE}$  is **constant and no lower than the  $V_{BE}$** , i.e.  $V_{CE} > V_{BE}$ . Thus, the BJT is in the forward active mode.

$I_C$  is independent of  $V_{CE}$ ; thus, different values of  $V_{CE}$  do not alter the characteristic.

$$i_C = I_S [e^{v_{BE}/V_T} - 1]$$
 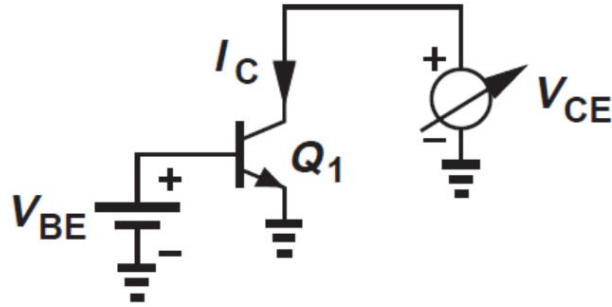
## IV characteristics – Output characteristic



**Output characteristic** shows  $I_C$  for a given  $V_{BE}$  but with  $V_{CE}$  varying.


$V_{CE} < V_{BE}$ , Both diodes (B-E and C-B) are on and thus the BJT is in a saturation.

$V_{CE} > V_{BE}$ , BJT is in a forward active.  $V_{BE}$  increases  $I_C$  increases as  $i_C = I_S [e^{v_{BE}/V_T} - 1]$
 
## Transconductance

In the **forward active region**, the transistor becomes a **better amplifying device** by producing larger changes in  $I_C$  in response to a given signal level ( $V_{BE}$ ) applied ( $I_C/V_{BE}$ ).

$g_m = dI_C / dV_{BE}$  represents the slope of  $I_C$ – $V_{BE}$  characteristic at a given  $I_{C0}$ , and the corresponding  $V_{BE0}$ . In other words, if  $V_{BE}$  experiences a small perturbation  $\pm \Delta V$  around  $V_{BE0}$ , then the  $I_C$  displays a change of  $\pm g_m \Delta V$  around  $I_{C0}$ .




$$\begin{aligned} g_m &= \frac{dI_C}{dV_{BE}} = \frac{d}{dV_{BE}} \left( I_S \exp \frac{V_{BE}}{V_T} \right) \\ &= \frac{1}{V_T} I_S \exp \frac{V_{BE}}{V_T} = \frac{I_C}{V_T} \end{aligned}$$




# Small-Signal Model

Without Early Effect

 


$$g_m = \frac{dI_C}{dV_{BE}} = \frac{I_C}{V_T}$$
 
$$r_\pi = \frac{\Delta V_{BE}}{\Delta I_B} = \frac{\beta}{g_m}$$




$\Rightarrow$   
DC off

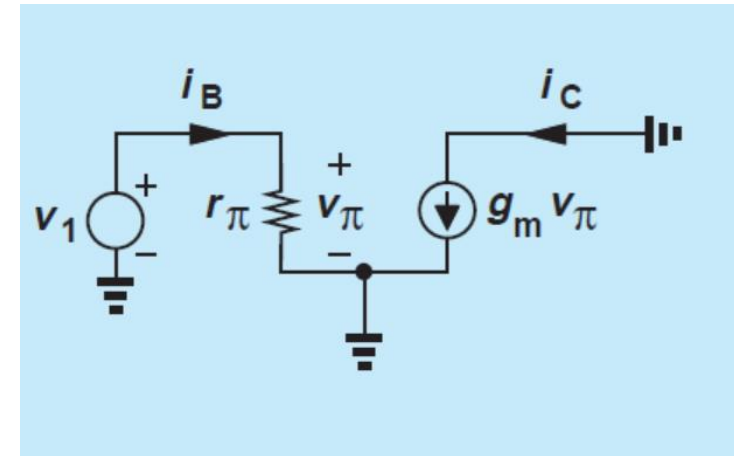

Ground all constant voltage sources and open all constant current sources while constructing the small-signal equivalent circuit


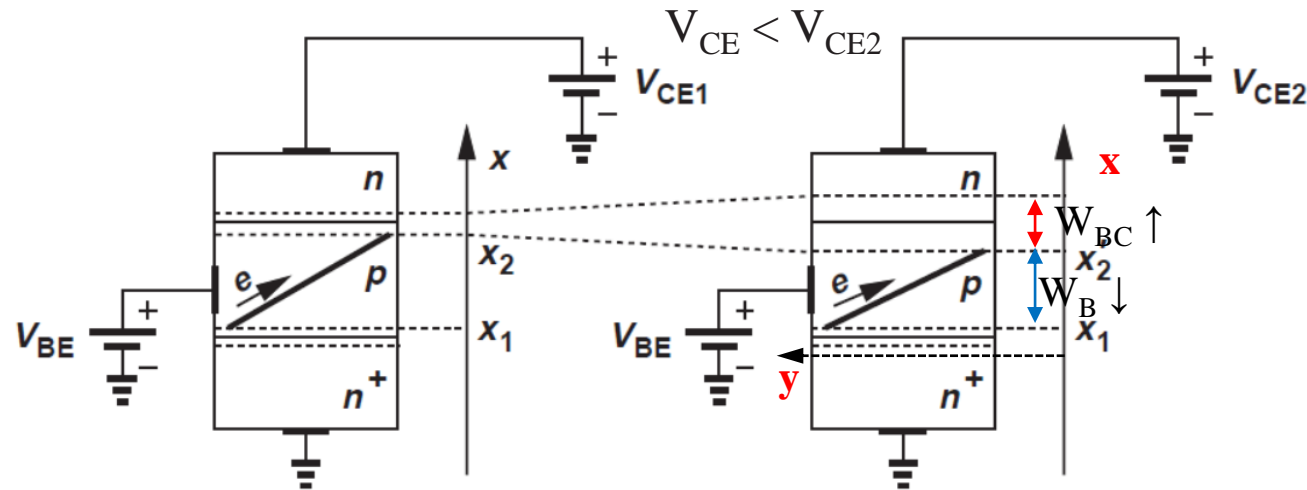
## Early Effect

As  $V_{CE} < V_{CE2}$ , the depletion region in C-B areas increases, and thus **the slope of the profile increases**. Equivalently, the effective  $W_B$  **decreases**, thereby **increasing  $I_C$** . Early effect indicates that the  $V_{CE}$  **does affect the  $I_C$** .





With the Early effect,  $I_C \approx \left( I_S \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$   $V_A = \text{Early voltage}$

  
Without the Early effect,  $i_C = I_S [e^{v_{BE}/V_T} - 1]$



  With the Early effect,  $I_C \approx \left( I_S \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$




## Small-signal model with Early effect


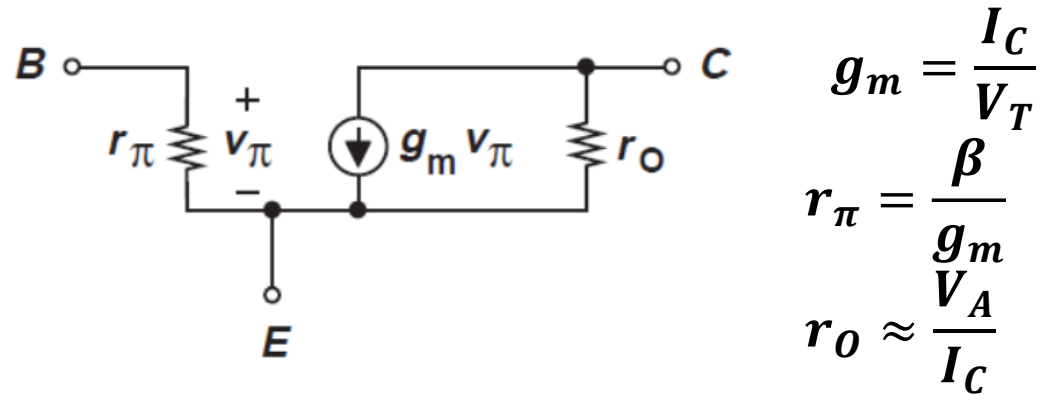


The small-signal model contains **only one extra element  $r_o$**  to represent the **Early effect**. This **output resistance  $r_o$**  plays a critical role in high gain amplifiers


# Summary

 



Without Early Effect

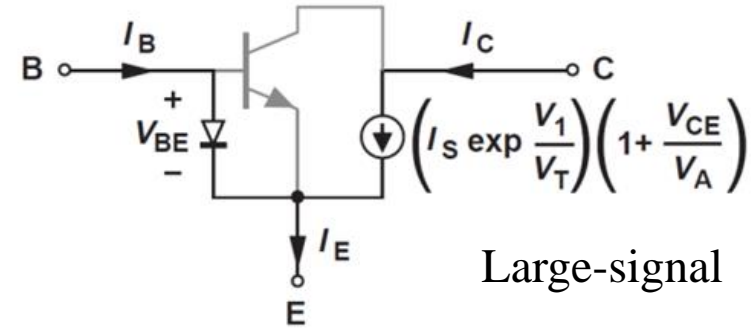 

With Early Effect

 

## PNP BJT

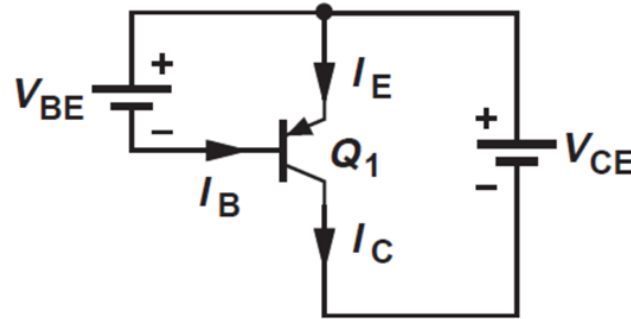 



$$i_C = i_F = I_S [e^{v_{EB}/V_T} - 1]$$

$$i_B = i_F / \beta_F = I_S / \beta_F [e^{v_{EB}/V_T} - 1]$$

$$i_E = \left( I_S + \frac{I_S}{\beta_F} \right) [e^{v_{EB}/V_T} - 1]$$

**Operation of PNP in the active region** requires forward biasing the base-emitter junction and reverse-biasing the collector junction. Thus,  $V_{BE} < 0$  (**Forward**) and  $V_{BC} > 0$  (**Reverse**). All of the operation principles and equations described for npn transistors apply to pnp devices as well.

## PNP BJT Small Signal model

 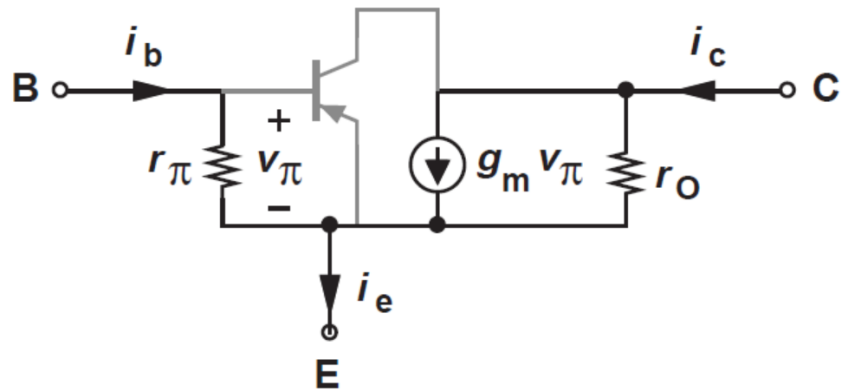


Since the small-signal model represents changes in the voltages and currents, we expect npn and pnp transistors to have similar models. **The small signal model of the pnp transistor is indeed identical to that of the npn device.**






## DC and Small-Signal Analysis

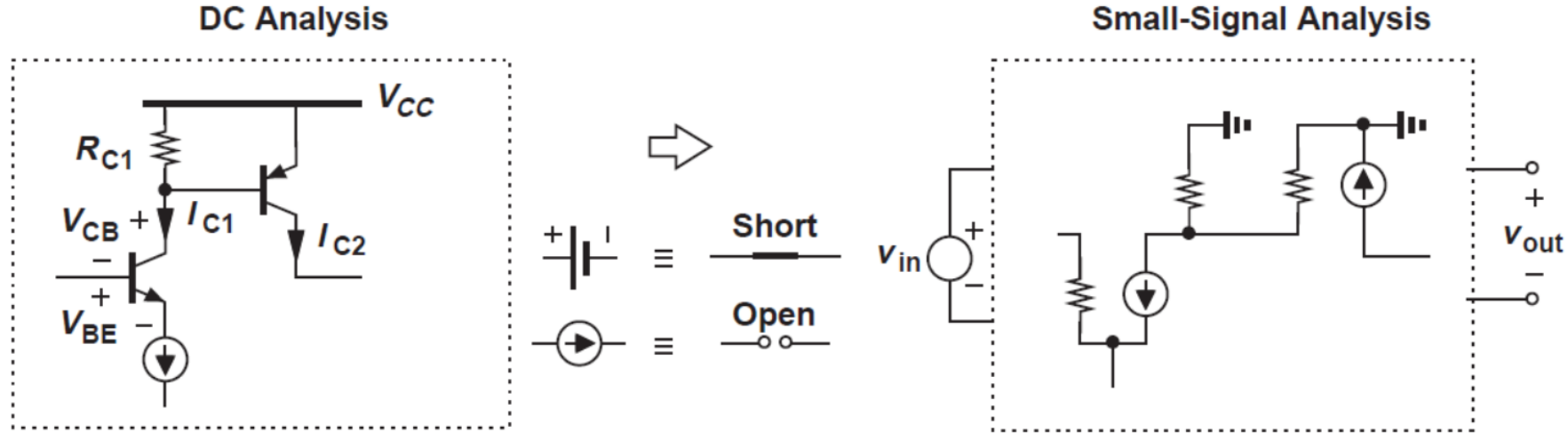


How to analyze a BJT circuit? (1) we determine the **effect of constant voltages and currents while signal sources are set to zero**; (2) we analyze the response to signal sources while **constant sources are set to zero**.

## Common-Emitter (C-E) Amplifier

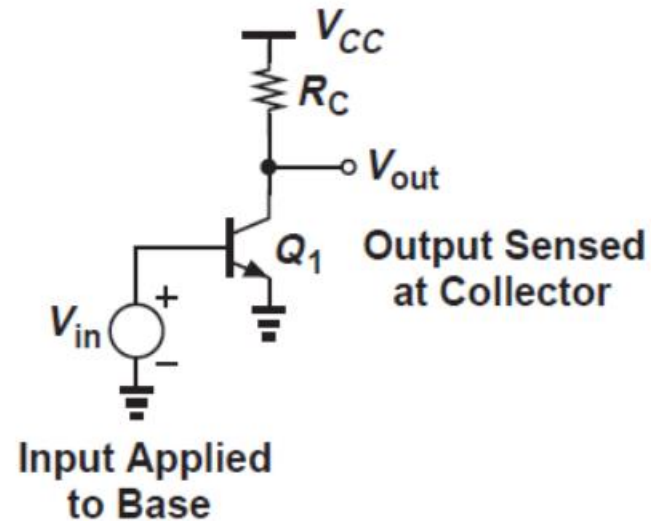

If the input signal is applied to base (B) and the output signal is sensed at the collector (C), the circuit is called a **common-emitter (C-E) stage**, i.e. **emitter (E) is grounded and appears in common to the input and output.**
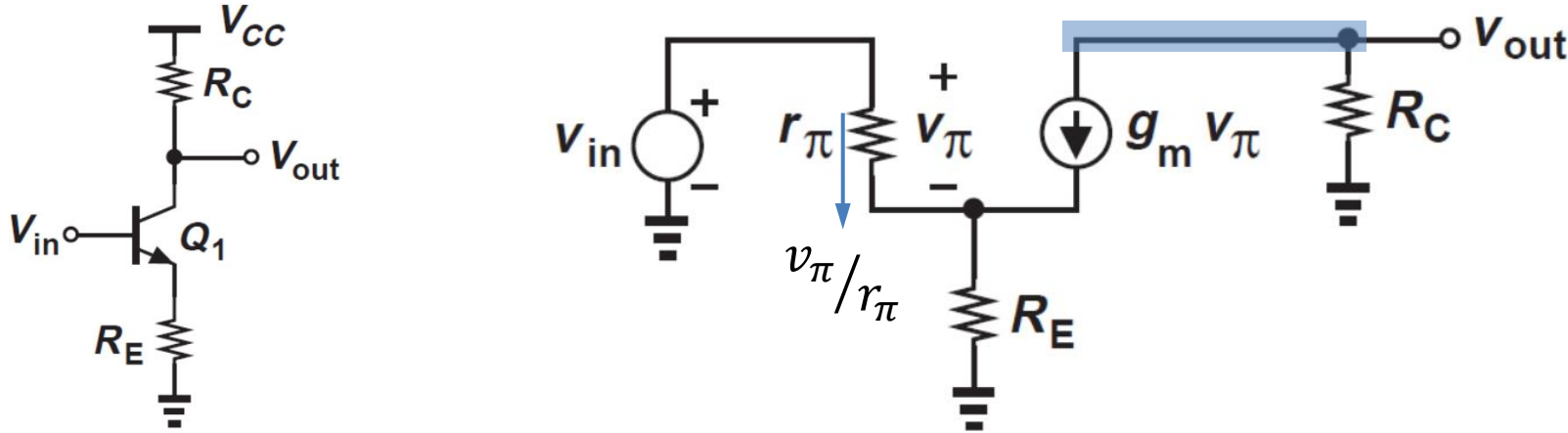
## CE Stage With Emitter Degeneration (Without Early Effect)



By KCL,  $-g_m v_\pi = v_{out}/R_C \rightarrow v_\pi = -v_{out}/g_m R_C$


Current through  $R_E = v_\pi/r_\pi + g_m v_\pi$

By KVL:  $-v_{in} + v_\pi + v_{R_E} = 0$  where  $v_{R_E} = (v_\pi/r_\pi + g_m v_\pi)R_E$

Thus,  $v_{in} = v_\pi + (v_\pi/r_\pi + g_m v_\pi)R_E = v_\pi [1 + (1/r_\pi + g_m)R_E]$

$$\frac{v_{out}}{v_{in}} = -\frac{g_m R_C}{1 + (1/r_\pi + g_m)R_E} \approx -\frac{g_m R_C}{1 + g_m R_E}$$

 
## CE Stage With Emitter Degeneration-Input and Output Impedance



$$v_\pi = r_\pi i_x$$



**Current through  $R_E$**  is  $i_x + g_m v_\pi = i_x + g_m r_\pi i_x = (1 + \beta) i_x$  as  $r_\pi = \beta / g_m$
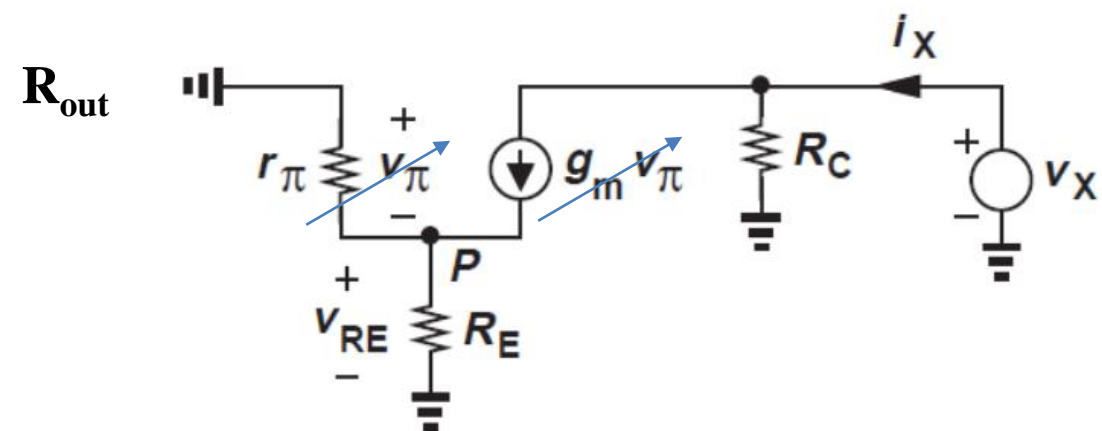
$$v_x = r_\pi i_x + R_E (1 + \beta) i_x \text{ and thus } R_{in} = v_x / i_x = r_\pi + (\beta + 1) R_E$$



$v_\pi = 0$ , all  $i_x$  flows through  $R_C$  and thus  $R_{out} = R_C$
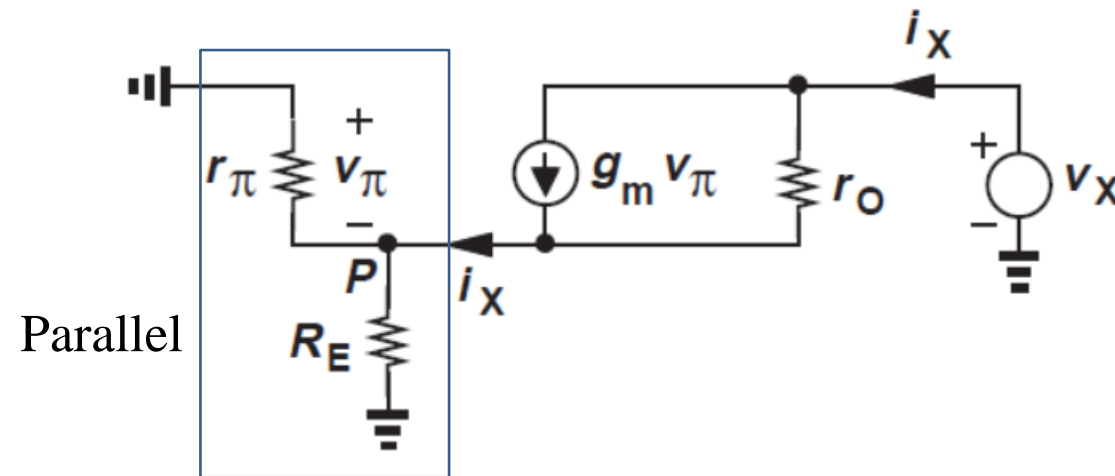 
## Effect of Transistor Output Resistance with Early Effect



$$v_\pi = -i_X(R_E \parallel r_\pi)$$

A current through  $r_o$  is  $i_X - g_m v_\pi$

By KVL:  $-v_X + r_o(i_X - g_m v_\pi) - v_\pi = 0 \rightarrow v_X = r_o[i_X + g_m i_X(R_E \parallel r_\pi)] + i_X(R_E \parallel r_\pi)$



$$R_{out} = v_X / i_X = r_o[1 + g_m(R_E \parallel r_\pi)] + (R_E \parallel r_\pi) \rightarrow r_o + (g_m r_o + 1)(R_E \parallel r_\pi)$$

$$R_{out} \approx r_o[1 + g_m(R_E \parallel r_\pi)] \text{ as } g_m r_o \gg 1 \text{ (intrinsic gain)}$$

**Increase in the output impedance  $r_o$  produces amplifiers with a higher gain.**

## Coupling capacitor




*↳ separate DC and AC signal.*

 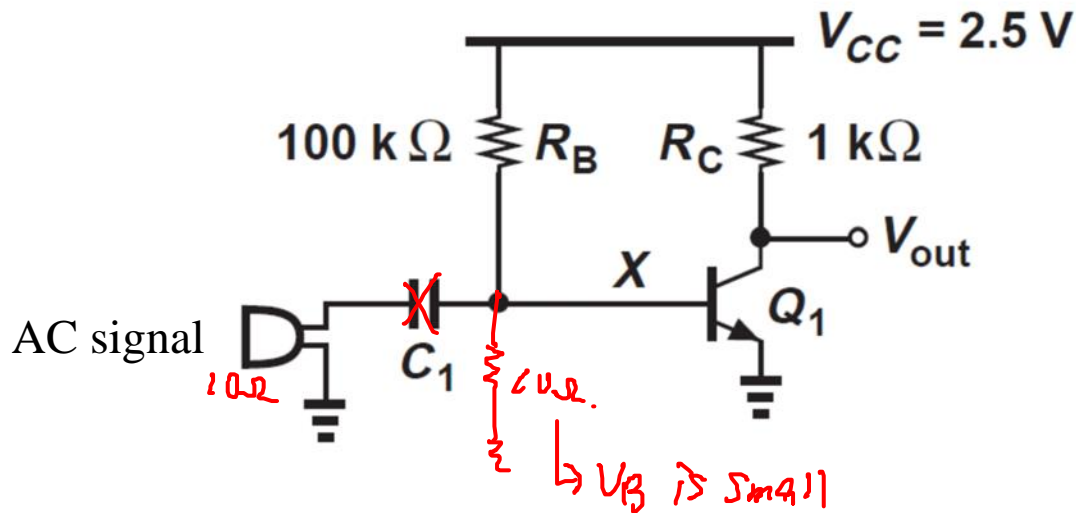

**A series capacitor** can be inserted to **isolate the dc biasing of the amplifier from the AC signal**.

The bias point of  $Q_1$  remains independent of the resistance of the microphone (AC signal) because  **$C_1$  carries no bias current (DC Open)**. The value of  $C_1$  is chosen so that it provides a relatively low impedance for the frequencies of interest (**AC Short**).  $C_1$  is a **coupling capacitor** and the input of this stage is **ac-coupled** or **capacitively coupled**.

e.g.

  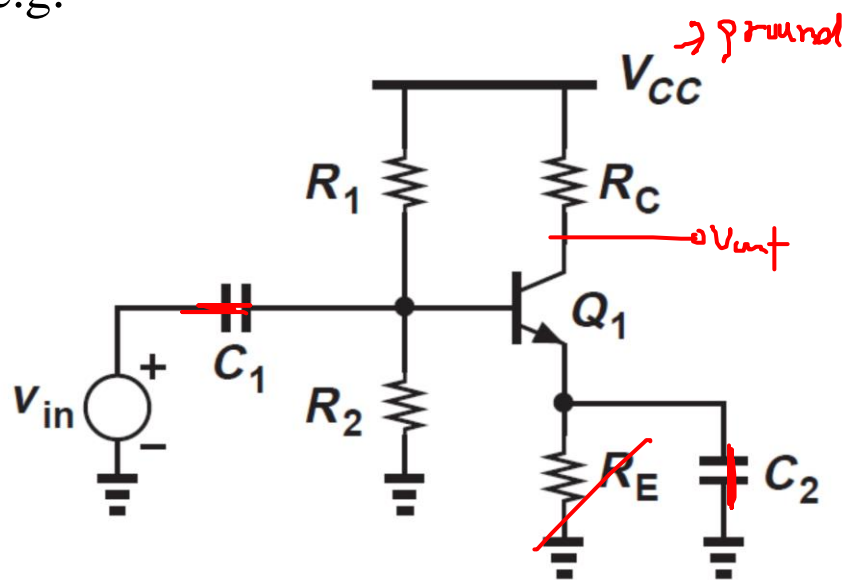


$$\frac{v_{out}}{v_{in}} = -g_m R_C$$

$$R_{in} = r_{\pi} \parallel R_1 \parallel R_2$$

$$R_{out} = R_C$$





## Common-Base (CB) Topology

 

**The input is applied to the emitter and the output is sensed at the collector.** Biased at a proper voltage, **the base acts as ac ground** and hence as a node “common” to the input and output ports.

## General case of the CB topology

Without Early effect

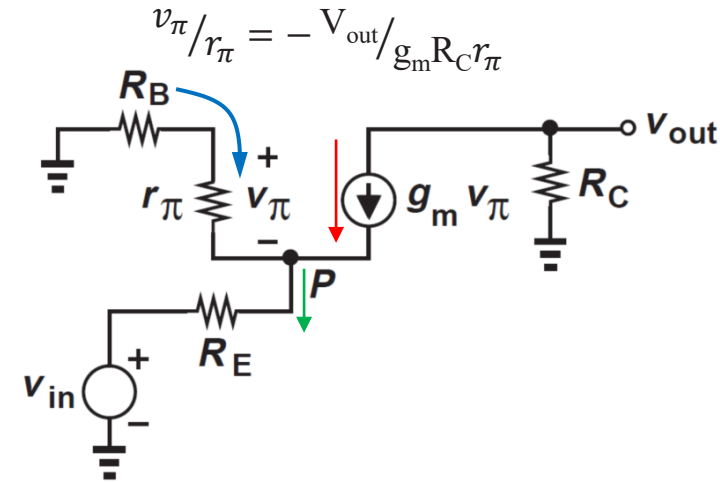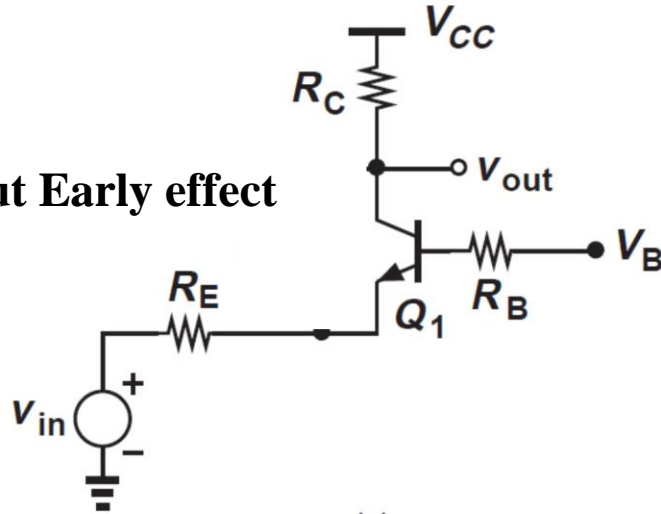


$$v_{out} = -g_m v_{\pi} R_C \rightarrow v_{\pi} = -v_{out} / g_m R_C$$

The current through the  $v_{\pi}$  node is  $v_{\pi} / r_{\pi} = -v_{out} / g_m R_C r_{\pi}$

Therefore, voltage at node p is  $v_p = v_{out} / g_m R_C r_{\pi} (R_B + r_{\pi}) = v_{out} / \beta R_C (R_B + r_{\pi})$  \*  $r_{\pi} = \frac{\beta}{g_m}$

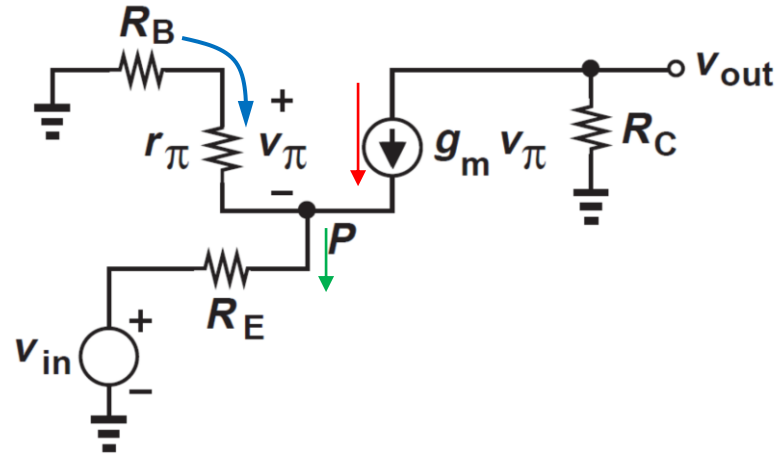KCL at node P, we get  $\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \frac{v_p - v_{in}}{R_E}$




KCL at node P, we get  $\frac{v_\pi}{r_\pi} + g_m v_\pi = \frac{v_p - v_{in}}{R_E}$  (1)

where  $v_\pi = -v_{out}/g_m R_C$  and  $v_p = -v_{out}/\beta R_C (R_B + r_\pi)$ .

Put  $v_\pi$  and  $v_p$  into the equation (1) and rearrange terms, we get

$$\frac{v_{out}}{v_{in}} = \frac{\beta R_C}{(\beta + 1)R_E + R_B + r_\pi} \text{ or } \approx \frac{R_C}{R_E + \frac{R_B}{\beta + 1} + \frac{1}{g_m}}$$
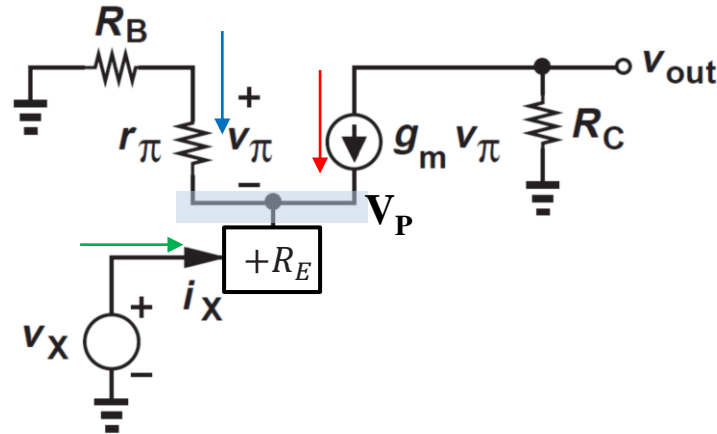
## Input Resistance of General CB Topology



$$-v_{\pi} = \frac{r_{\pi}}{R_B + r_{\pi}} v_p, v_p = v_x - R_E i_x$$

KCL at node P gives  $\frac{v_{\pi}}{r_{\pi}} + i_x + g_m v_{\pi} = 0$


This results in  $\left(\frac{1}{r_{\pi}} + g_m\right) v_{\pi} + i_x = 0$  where  $-v_{\pi} = \frac{r_{\pi}}{R_B + r_{\pi}} (v_x - R_E i_x)$

$$\left(\frac{1}{r_{\pi}} + g_m\right) \frac{r_{\pi}}{R_B + r_{\pi}} (v_x - R_E i_x) = i_x \quad *r_{\pi} = \frac{\beta}{g_m}$$

$= 1 + \beta$

Rearrange terms we get  $\frac{v_x}{i_x} = R_E + \frac{R_B + r_{\pi}}{\beta + 1}$  or without  $R_E$  (series R)  $\frac{v_x}{i_x} = \frac{R_B}{\beta + 1} + \frac{1}{g_m}$

## Emitter Follower

 


In an emitter follow circuit,  $V_{out}$  is always lower than  $V_{in}$  by an amount equal to  $V_{BE}$ , and the circuit is said to provide **level shift** and a **voltage gain less than unity**.

Even though the voltage gain is less than unity, the **input and output impedances** of the emitter follower make it a particularly useful circuit for some applications.

With Early effect

(1) Gain

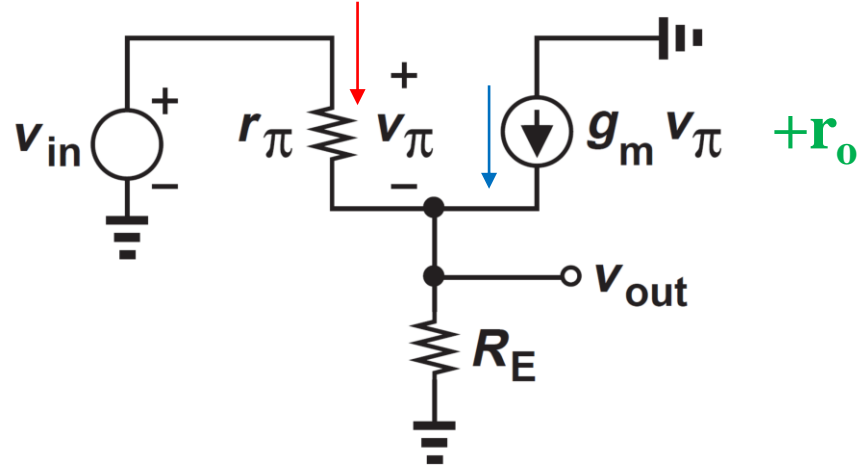

By small signal analysis, the equivalent circuit yields

$$\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \frac{v_{out}}{R_E} + \frac{v_{out}}{r_o}$$


$$v_{\pi} = \frac{r_{\pi}}{\beta + 1} \cdot \frac{v_{out}}{R_E \parallel r_o}$$

$$v_{in} = v_{\pi} + v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + \frac{r_{\pi}}{\beta + 1} \cdot \frac{1}{R_E \parallel r_o}} \approx \frac{R_E \parallel r_o}{R_E \parallel r_o + \frac{1}{g_m}}$$

With Early effect

## (2) Input Impedances

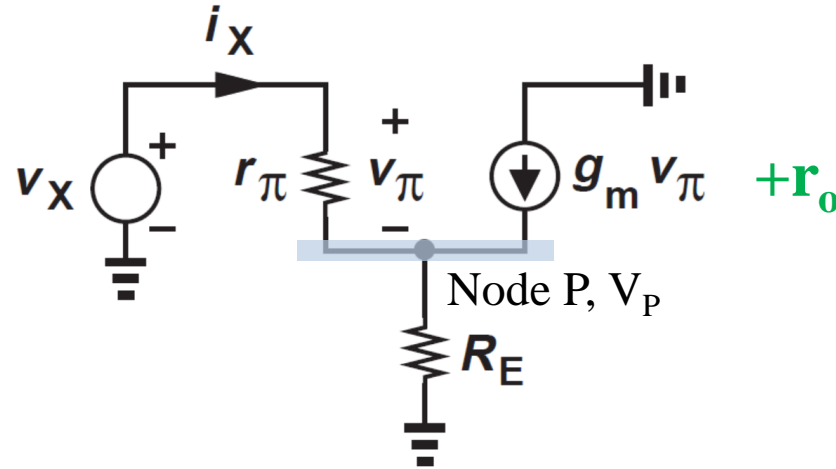

From the circuit above, we can derive



$$v_\pi = i_X r_\pi; V_P = v_X - v_\pi = v_X - i_X r_\pi$$

By KCL at node P,  $i_X + g_m v_\pi = \frac{V_P}{R_E} + \frac{V_P}{r_o}$  where  $\frac{1}{R_E} + \frac{1}{r_o} = \frac{1}{R_E \parallel r_o}$

$$\rightarrow R_{in} = \frac{v_X}{i_X} = (1 + g_m r_\pi)(R_E \parallel r_o) + r_\pi = (1 + \beta)(R_E \parallel r_o) + r_\pi$$

With Early effect

### (3) Output Impedances

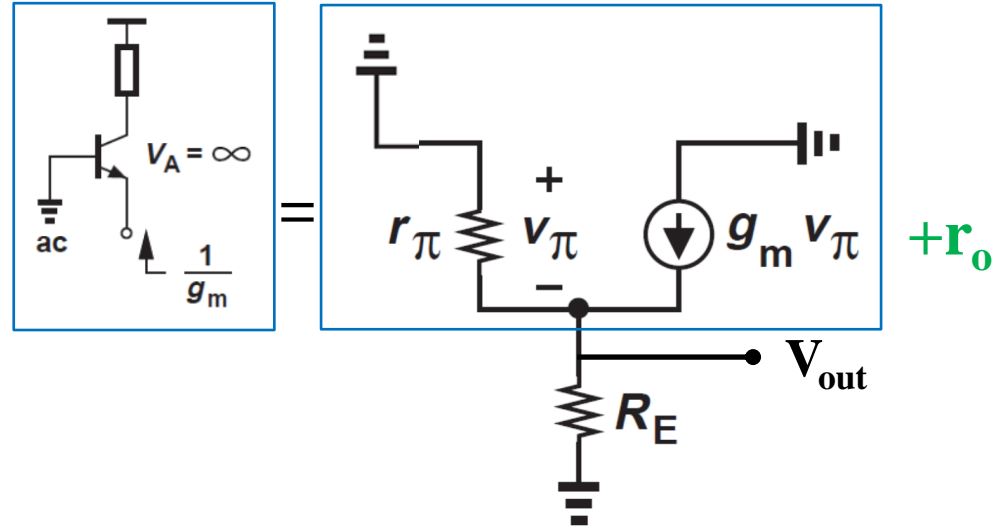 




$$R_{out} = \frac{1}{g_m} \parallel R_E \parallel r_o$$




   
# MOS I/V Characteristics

Assume we change  $V_G$  from negative to positive




**Electron direction**


**Drain current ( $I_D$ ) direction**

- By applying **positive**  $V_{GS}$ , electrons are induced in the channel, or holes are repelled from the channel, forming a **depletion region** at the interface between oxide and Si.
- When  $V_{GS}$  ( $> 0$ ) is large enough, a **channel of electrons (inversion layer)** is formed at the interface.
- The value of  $V_{GS}$  at which the inversion layer forms is the **threshold voltage ( $V_{TH}$ )**. The device turns on abruptly for  $V_{GS} \geq V_{TH}$ .
- **With the bias of  $V_{DS}$ , electrons flow from source to drain.**

## Threshold Voltage (PMOS)

 

 
**Hole and drain current ( $I_D$ ) direction**




The turn-on phenomenon in a PMOS device is similar to that of NFETs, but with all the polarities reversed. If the  $V_{GS}$  becomes sufficiently *negative*, an inversion layer consisting of holes is formed at the oxide-silicon interface, providing a conduction path between the source and the drain.  $V_{TH}$  of PMOS  $< 0$ .

## Modes of MOSFET

 - (1)  $V_{GS} < V_{TH}$ : No channel exists, the **device is off**, and  $I_D = 0$  regardless of the value of  $V_{DS}$ .
- (2)  $V_{GS} > V_{TH}$ : The channel is formed. With  $V_{DS} > 0$ , the **device is on** and there is  $I_D > 0$ .




MOSFET Bias:  $V_{GS}$  and  $V_{DS}$

 

Transfer curve

By varying  $V_{GS}$  at fixed  $V_{DS}$

 


Output curve

By varying  $V_{DS}$  at fixed  $V_{GS}$


In an output curve of MOSFET, we can determine two modes (regions): (1) **Triode or ohmic region** and (2) **saturation region**.

## Saturation Region

 


When the  $V_{DS} > V_{GS} - V_{TH}$ , the drain current does not follow the parabolic behavior. In fact,  $I_D$  becomes relatively constant and the device operates in the **saturation region**.

 $V_{DS} = V_{GS} - V_{TH}$  is the minimum value for the NMOS to operate in saturation region.  
For  $V_{DS} > V_{GS} - V_{TH}$ ,  $I_D$  becomes relatively constant.



The local density of the inversion-layer charge is proportional to  $V_{GS} - V(x) - V_{TH}$ . Thus, if  $V(x)$  approaches  $V_{GS} - V_{TH}$ , then  $Q_d(x)$  drops to zero. In other words, if  $V_{DS}$  is slightly greater than  $V_{GS} - V_{TH}$ , then the inversion layer stops at  $x \leq L$ , and the channel is **pinched off**. As  $V_{DS}$  increases further, **the point at which  $Q_d$  equals zero gradually moves toward the source**.

 


When  $V_{DS} = V_{GS} - V_{TH}$ , the saturation occurs. Thus, substitute  $V_{DS}$  with  $V_{GS} - V_{TH}$  then

$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} [(V_{GS} - V_{TH})V_{DS} - \frac{1}{2} V_{DS}^2] \rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$


$L'$ : the point at which  $Q_d$  drops to zero

## NMOS vs PMOS

 

Triode region:  $I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$

 Saturation region:  $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$




Triode region:  $I_D = -\mu_p C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$

Saturation region:  $I_D = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$


 
## Transconductance


**Transconductance ( $g_m$ )** indicates how well a device converts a voltage to a current. Transconductance is usually defined in the saturation region.



$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH}) = \sqrt{2 \mu_n C_{ox} \frac{W}{L'} I_D} = \frac{2 I_D}{V_{GS} - V_{TH}}$$

## Second-Order Effects

### Body Effect

 

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|})$$

(-)


As  $V_B$  or  $V_{BS}$  becomes more negative ( $V_{SB} > 0$ ), more holes are attracted to the substrate connection, leaving a larger negative charge behind. the depletion region becomes wider.

More depletion charge (bound charge)  $Q_d \uparrow \rightarrow V_{TH}$  increases

$$V_{TH} = \Phi_{MS} + 2\Phi_F + \frac{Q_{dep}}{C_{ox}}$$

 **For the transconductance,**


$$\begin{aligned}
 g_{mb} &= \frac{\partial I_D}{\partial V_{BS}} (= -\frac{\partial I_D}{\partial V_{SB}}) = \frac{\partial I_D}{\partial V_{TH}} \cdot \frac{\partial V_{TH}}{\partial V_{BS}} \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \cdot \frac{\partial V_{TH}}{\partial V_{BS}} \\
 &= g_m \cdot \eta
 \end{aligned}$$



- $V_{GS}$  positively increases,  $I_D$  increases.
- $V_{BS}$  positively increases, i.e.  $V_{SB}$  negatively increases,  $V_{TH}$  decreases and thus  $I_D$  increases.
 
## Channel-Length Modulation

**The actual length of the channel gradually decreases** as the potential difference between the gate and the drain decreases.  $L$  is in fact a function of  $V_{DS}$ .



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L'} (V_{GS} - V_{TH})^2$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \left( 1 + \frac{\Delta L}{L_{eff}} \right)$$


$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

**With the channel-length modulation,**

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH}) (1 + \lambda V_{DS})$$

 
$$r_o = \frac{\partial V_{DS}}{\partial I_D} = 1 / \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda} \approx \frac{1}{I_D \cdot \lambda}$$




**Channel-length modulation is reflected in  $g_m$  and  $r_o$  by  $\lambda$**
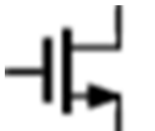
## Small-Signal Model for NMOS

$$\begin{aligned}
 V_d &= V_D + v_d \\
 V_g &= V_G + v_g \\
 V_s &= V_S + v_s
 \end{aligned}$$




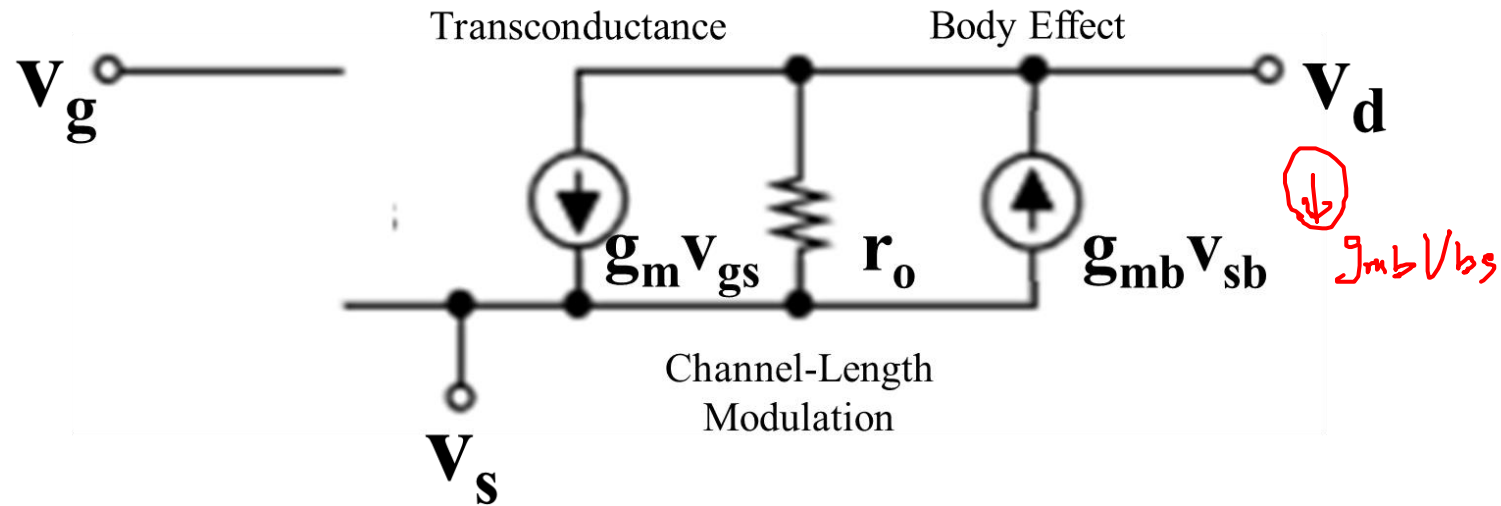$I_D$  (blue arrow pointing down)   
  $i_d = g_m v_{gs}$  (green)   
  $i_d = g_{mb} v_{sb}$  (red, arrow pointing up)   
  $i_d = g_{mb} v_{bs}$  (red, arrow pointing down)


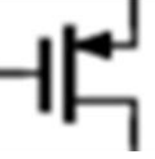
## Small-Signal Model for PMOS

$$\begin{aligned}
 V_s &= V_S + v_s \\
 V_g &= V_G + v_g \\
 V_d &= V_D + v_d
 \end{aligned}$$



$\downarrow I_D \uparrow i_d = g_m v_{gs} \quad \uparrow i_d = g_{mb} v_{sb}$

