

Question 1. MOSFET DC Biasing


[40 points] Use the drain current equations below. Don't consider channel-length modulation and body effect. Assuming $\mu_n = 350 \times 10^{-4} m^2/V/s$, $\mu_p = 350 \times 10^{-4} m^2/V/s$, $V_{TH} = 0.7V$ (NMOS), $V_{TH} = -0.8V$ (PMOS), $W_{drawn}/L_{drawn} = 20\mu m/2\mu m$, $t_{ox} = 9 \times 10^{-9} m$, $L_D = 0.08\mu m$, sketch I_X of M_1 as a function of V_X increasing from 0V to $V_{DD} = 5V$.

$$(1) \quad I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \text{ (NMOS in triode region)}$$

$$(2) \quad I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 \text{ (NMOS in saturation region)}$$

$$(3) \quad I_D = \mu_p C_{ox} \frac{W}{L_{eff}} \left[(V_{SG} - |V_{TH}|) V_{SD} - \frac{1}{2} V_{SD}^2 \right] \text{ (PMOS in triode region)}$$

$$(4) \quad I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L_{eff}} (V_{SG} - |V_{TH}|)^2 \text{ (PMOS in saturation region)}$$

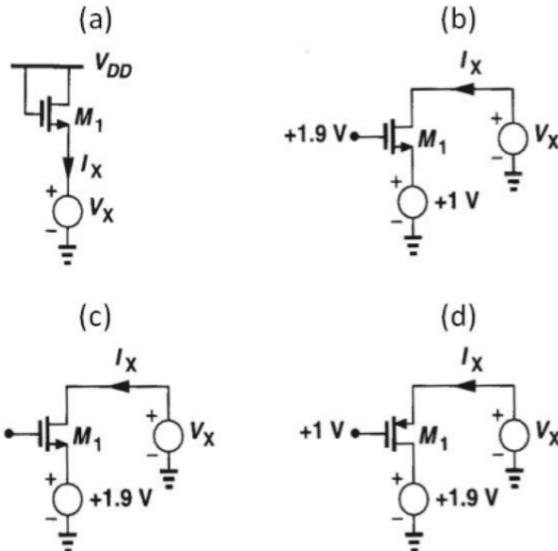

$$C_{ox} = \epsilon_{ox}/t_{ox} = 8.85 \times 10^{-12} \times 3.9 / 9 \times 10^{-9} = 3.835 \times 10^{-3} F/m^2$$


$$L_{eff} = L_{drawn} - 2L_D = 2 - 2 \times 0.08 = 1.84 \mu m$$

$$(a) \quad V_{GS} = V_{DS} = 5 - V_X$$

$$5 - V_X < V_{TN} = 0.7V \Rightarrow V_X > 4.3V, \text{ NMOS in cutoff, } I_X = 0$$

When $V_X < 4.3V$, $V_{DS} > V_{GS} - V_{TN}$, NMOS in saturation
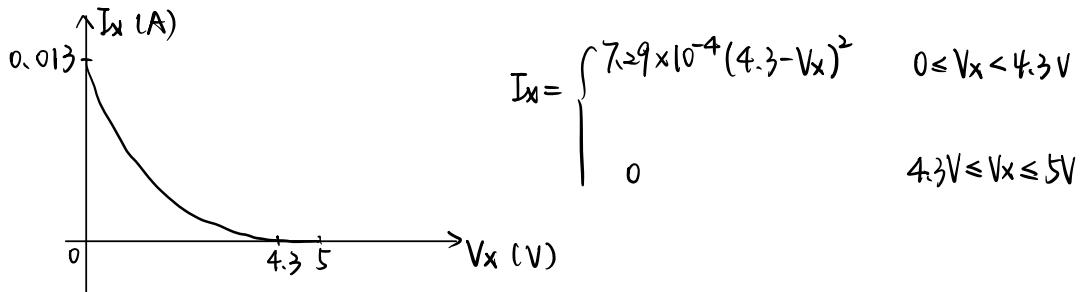
$$\begin{aligned} I_X &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TN})^2 \\ &= \frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} (5 - V_X - 0.7)^2 \\ &= 7.29 \times 10^{-4} (4.3 - V_X)^2 \end{aligned}$$



(b) ① $V_x > 1 V$

$$V_{GS} = 0.9 V, V_{DS} = V_x - 1$$

$$V_{GS} > V_{TN} \Rightarrow \text{on}$$

$$V_{DS} > V_{GS} - V_{TN} \Rightarrow V_x - 1 > 0.9 - 0.7 \Rightarrow V_x > 1.2 V, \text{ saturation}$$

(i) When $V_x > 1.2 V$, saturation

$$\begin{aligned} I_x &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TN})^2 \\ &= \frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} \times 0.2^2 \\ &= 2.92 \times 10^{-5} A \end{aligned}$$

(ii) When $1 V < V_x < 1.2 V$, triode

$$\begin{aligned} I_x &= \mu_n C_{ox} \frac{W}{L_{eff}} [(V_{GS} - V_{TN}) V_{DS} - \frac{1}{2} V_{DS}^2] \\ &= 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} [0.2(V_x - 1) - \frac{1}{2}(V_x - 1)^2] \\ &= 1.46 \times 10^{-3} (V_x - 1)(0.7 - 0.5V_x) \end{aligned}$$


② $V_x < 1 V$

$$V_{GS} = 1.9 - V_x, V_{DS} = 1 - V_x$$


$$V_{GS} > V_{TN} \Rightarrow \text{on}$$

$$V_{DS} < V_{GS} - V_{TN} = 1.9 - V_x - 0.7 = 1.2 - V_x \Rightarrow \text{triode}$$
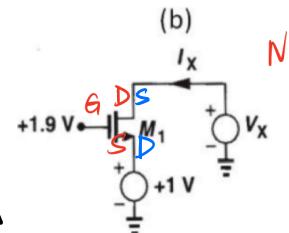
$$\begin{aligned} I_x &= -\mu_n C_{ox} \frac{W}{L_{eff}} [(V_{GS} - V_{TN}) V_{DS} - \frac{1}{2} V_{DS}^2] \\ &= -350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} [(1.2 - V_x)(1 - V_x) - \frac{1}{2}(1 - V_x)^2] \\ &= 1.46 \times 10^{-3} (V_x - 1)(0.7 - 0.5V_x) \end{aligned}$$



$$I_x$$

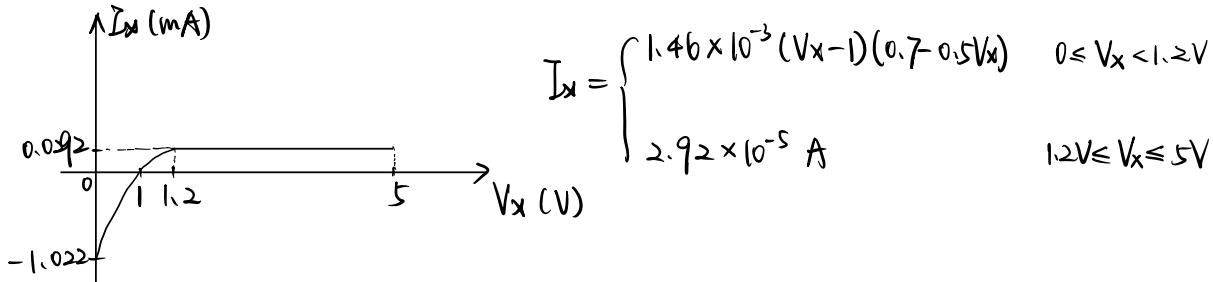

(c) ① $V_x > 1.9V$

$$V_{GS} = -0.9V < V_{TN} \Rightarrow \text{off}, I_x = 0$$


② $V_x < 1.9V$

$$V_{GS} = 1 - V_x, V_{DS} = 1.9 - V_x$$

$$V_{GS} = 1 - V_x < V_{TN} \Rightarrow V_x > 1 - V_{TN} = 0.3V \Rightarrow \text{off}, I_x = 0$$

$$(1) 0.3V < V_x < 1.9V, I_x = 0$$

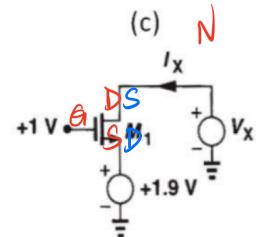
$$(2) 0 < V_x < 0.3V, V_{DS} > V_{GS} - V_{TN} = 1 - V_x - 0.7 = 0.3 - V_x \Rightarrow \text{saturation}$$



$$I_x = -\frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TN})^2$$

$$= -\frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} (0.3 - V_x)^2$$

$$= -7.29 \times 10^{-4} (0.3 - V_x)^2$$

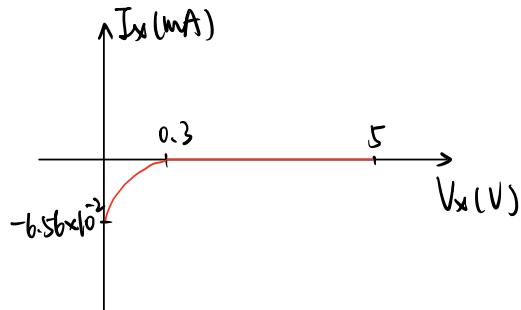

$$I_x = \begin{cases} -7.29 \times 10^{-4} (0.3 - V_x)^2 & 0 \leq V_x \leq 0.3V \\ 0 & 0.3V < V_x \leq 5V \end{cases}$$

$$0.3V < V_x \leq 5V$$

(d) ① $V_x > 1.9V$

$$V_{GS} = V_x - 1, V_{SD} = V_x - 1.9 \Rightarrow |V_{GS}| > |V_{TP}| \Rightarrow \text{on}$$

$$V_{SD} < V_{GS} - |V_{TP}| = V_x - 1 - 0.8 = V_x - 1.8 \Rightarrow \text{triode}$$

$$I_x = \mu_p C_{ox} \frac{W}{L_{eff}} [(V_{GS} - |V_{TP}|) V_{SD} - \frac{1}{2} V_{SD}^2]$$


$$= 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} [(V_x - 1.8)(V_x - 1.9) - \frac{1}{2}(V_x - 1.9)^2]$$

$$= 1.46 \times 10^{-3} (V_x - 1.9)(0.5V_x - 0.85)$$

② $V_x < 1.9V$

$$V_{GS} = 1.9 - 1 = 0.9V, V_{SD} = 1.9 - V_x \Rightarrow |V_{GS}| > |V_{TP}| \Rightarrow \text{on}$$

$$V_{SD} > V_{GS} - |V_{TP}| \Rightarrow 1.9 - V_x > 0.9 - 0.8 = 0.1 \Rightarrow V_x < 1.8V, \text{saturation}$$

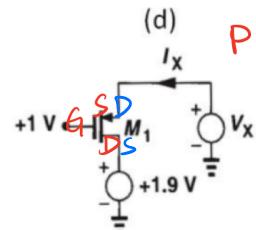

(1) $V_X < 1.8V \Rightarrow$ saturation

$$I_X = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L_{eff}} (V_{SD} - |V_{TP}|)^2$$

$$= -\frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} (0.9 - 0.8)^2$$


$$= -7.26 \times 10^{-6} A$$

(2) $1.8V < V_X < 5V \Rightarrow$ triode

$$I_X = -\mu_p C_{ox} \frac{W}{L_{eff}} [(V_{SD} - |V_{TP}|) V_{SD} - \frac{1}{2} V_{SD}^2]$$


$$= -350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20}{1.84} [0.1 (1.9 - V_X) - \frac{1}{2} (1.9 - V_X)^2]$$

$$= 1.46 \times 10^{-3} (V_X - 1.9)(0.5V_X - 0.85)$$

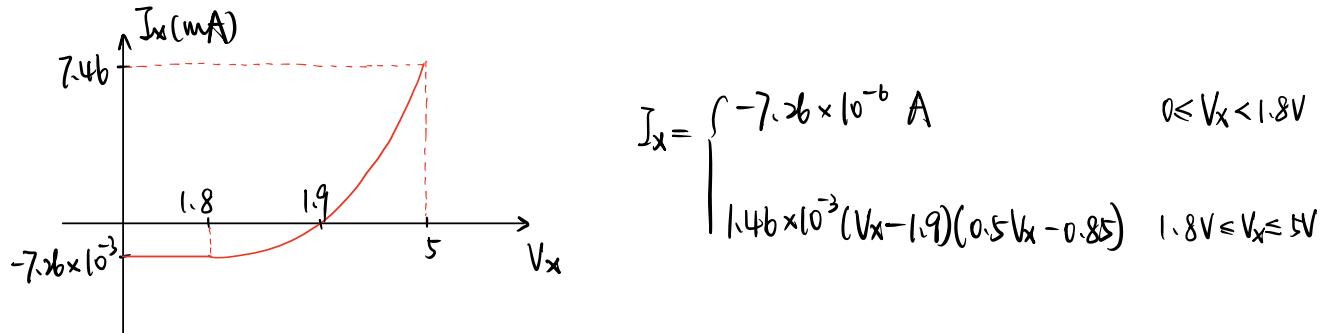

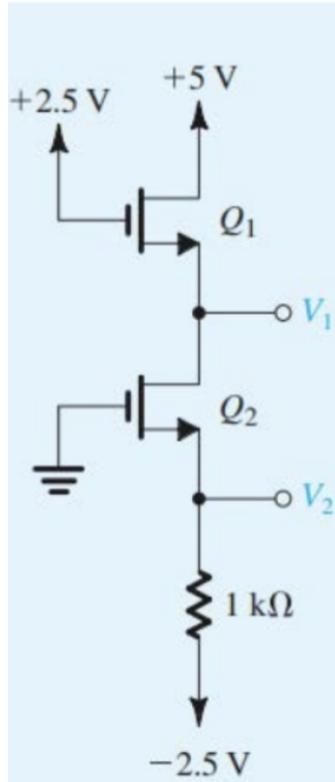Question 2. Combination of MOSFET

[10 points] For the circuit below, find the labeled node voltages. The NMOS transistor has $V_{TH} = 0.9V$, $k_n = \mu_n C_{ox}(W/L) = 1.5mA/V^2$.



$$V_{GS1} = 2.5 - V_1, \quad V_{DS1} = 5 - V_1, \quad V_{GS2} = -V_2, \quad V_{DS2} = V_1 - V_2 \Rightarrow V_{DS1} > V_{GS1} - V_{TH}$$

Assume Q_1, Q_2 both in saturation

$$\begin{cases} I_D = \frac{1}{2} k_n (V_{GS1} - V_{TH})^2 = \frac{1}{2} k_n (2.5 - V_1 - 0.9)^2 = \frac{1}{2} k_n (1.6 - V_1)^2 \\ I_D = \frac{1}{2} k_n (V_{GS2} - V_{TH})^2 = \frac{1}{2} k_n (-V_2 - 0.9)^2 \\ V_2 + 2.5 = 10^3 \cdot I_D \end{cases}$$

$$\Rightarrow V_2 = 1.37V \text{ or } -1.84V \Rightarrow V_2 = -1.84V \text{ since } V_{GS2} > V_{TH} \text{ in saturation}$$



$$\Rightarrow V_1 = 0.66V \text{ or } 2.54V \Rightarrow V_1 = 0.66V \text{ since } V_{GS1} > V_{TH} \text{ in saturation}$$

$$V_{DS2} = 0.66 + 1.84 = 2.5V, \quad V_{GS2} = 1.84V \Rightarrow V_{DS2} > V_{GS2} - V_{TH} \Rightarrow \text{Assumption satisfied.}$$

So $V_1 = 0.66V, V_2 = -1.84V$.

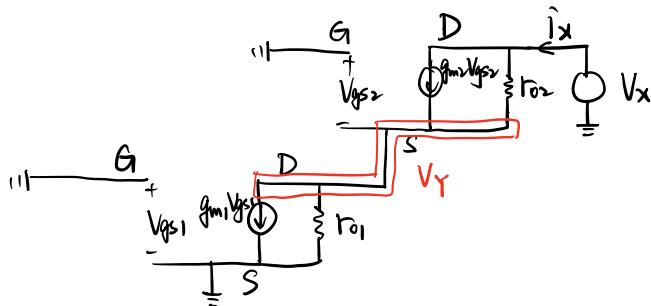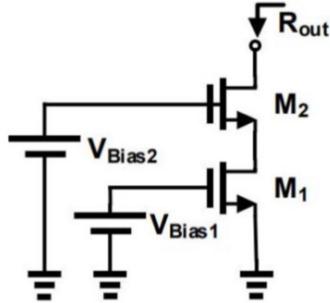Question 3. Small Signal of of MOSFET

[10 points] The circuit shown below is a MOSFET cascode amplifier. Draw the small signal model and derive R_{out} for the amplifier. Assume transistors M_1 and M_2 are in saturation and include r_O in your calculation.




$$\left\{ \begin{array}{l} V_{gs1} = 0 , V_{gs2} = -V_Y \\ \frac{V_Y}{r_{O1}} - i_x = 0 \\ V_Y = V_x - r_{O2}(i_x - g_{m2}V_{gs2}) \end{array} \right.$$

$$\Rightarrow \begin{aligned} r_{O1}i_x &= V_x - r_{O2}i_x - g_{m2}V_Y r_{O2} \\ r_{O1}i_x &= V_x - r_{O2}i_x - g_{m2}r_{O1}r_{O2}i_x \\ V_x &= (r_{O1} + r_{O2} + g_{m2}r_{O1}r_{O2})i_x \\ R_{out} &= \frac{V_x}{i_x} = r_{O1} + r_{O2} + g_{m2}r_{O1}r_{O2} \end{aligned}$$

So R_{out} = r_{O1} + r_{O2} + g_{m2}r_{O1}r_{O2}.

Question 4. Common-Source with Resistive Load

[20 points] Assume $\lambda = 0$ and $\gamma = 0$. For $V_{DD} = 5V$, $V_{in} = 0.9 V + \text{small signal}$, $R_D = 15k\Omega$ and $L_{drawn} = 2\mu m$, find out the value W_{drawn} to obtain a voltage gain $|A_v| > 10$ and V_{OUT} (the DC biasing voltage at the output) close to 2.5 V as much as possible.

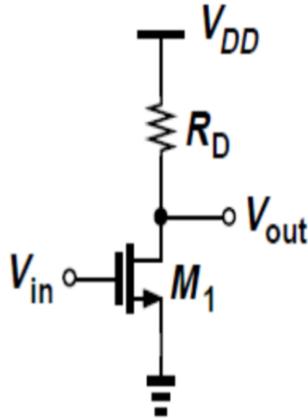

$$DC: V_{GS} = V_{IN} = 0.9 V, V_{TN} = 0.7 V, V_{DS} = V_{OUT} = 2.5 V$$

Assume saturation region.

$$\begin{aligned} \frac{V_{DD} - V_{out}}{R_D} &= I_D = \frac{1}{2} \mu n C_{ox} \frac{W_{drawn}}{L_{drawn} - 2L_D} (V_{GS} - V_{TN})^2 \\ \Rightarrow W_{drawn} &= \frac{2(V_{DD} - V_{out})(L_{drawn} - 2L_D)}{R_D \mu n C_{ox} (V_{GS} - V_{TN})^2} \\ &= \frac{2 \times (5 - 2.5)(2 - 2 \times 0.08)}{15 \times 10^3 \times 350 \times 10^{-4} \times \frac{8.85 \times 10^{-12} \times 3.9}{9 \times 10^{-9}} \times (0.9 - 0.7)^2} \\ &= 114.24 \mu m. \end{aligned}$$

$$AC: |A_v| = \left| \frac{V_{out}}{V_{in}} \right| = g_m R_D = \mu n C_{ox} \frac{W_{drawn}}{L_{drawn} - 2L_D} (V_{GS} - V_{TN}) R_D > 10$$

$$W_{drawn} > \frac{10(L_{drawn} - 2L_D)}{\mu n C_{ox} R_D (V_{GS} - V_{TN})} = \frac{10(2 - 2 \times 0.08)}{350 \times 10^{-4} \times \frac{8.85 \times 10^{-12} \times 3.9}{9 \times 10^{-9}} \times (0.9 - 0.7) \times 15 \times 10^3} = 45.69 \mu m$$


So $W_{drawn} = 114.24 \mu m$.

Question 5. CS Stage DC & AC Analysis

[20 points] In the circuit below, assume $\lambda = \gamma = 0$, $\mu_n C_{ox} \left(\frac{W}{L}\right)_1 = 1mA/V^2$, $\mu_p C_{ox} \left(\frac{W}{L}\right)_2 = 5mA/V^2$, $V_{TN} = 0.7V$, $V_{TP} = -1V$, $I_{D1} = I_{D2} = 0.5mA$, $V_{DD} = 5V$, $V_b = 1V$.

(a) Calculate V_{IN} and R_D so that M_1 is at the edge of saturation.

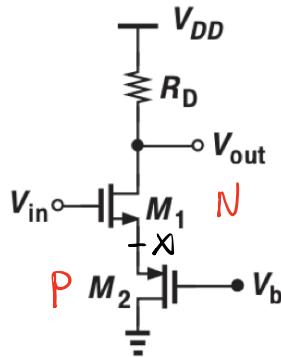(b) Derive the voltage gain $A_v = \frac{v_{out}}{v_{in}}$ of the circuit.



(a) $M_2: V_D < V_b + |V_{TP}| \Rightarrow M_2$ always in saturation.

$$\begin{aligned} I_{D2} &= \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_X - V_b - |V_{TP}|)^2 \\ &= \frac{1}{2} \cdot 5m (V_X - 1 - 1)^2 \\ &= 0.5mA \end{aligned}$$

$$\Rightarrow V_X = 1.55V \text{ or } 2.45V$$

For M_2 to be in saturation, $V_X > V_b + |V_{TP}| = 1 + 1 = 2V$

$$\therefore V_X = 2.45V$$

$$\begin{aligned} I_{D1} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_X - V_{TN})^2 \\ &= \frac{1}{2} \cdot 1m (V_{in} - 2.45 - 0.7)^2 \\ &= 0.5mA \end{aligned}$$

$$\Rightarrow V_{in} = 4.15V \text{ or } 2.15V$$

For M_1 to be in saturation, $V_{in} > V_X + V_{TN} = 2.45 + 0.7 = 3.15V$

$$\therefore V_{in} = 4.15V$$

M_1 is at the edge of saturation: $V_{out} = V_{in} - V_{TN} = 3.45V$


$$\therefore R_D = \frac{V_{DD} - V_{out}}{I_{D1}} = \frac{5 - 3.45}{0.5 \text{ mA}} = 3.1 \text{ k}\Omega$$

$$\therefore V_{IN} = 4.15 \text{ V}, R_D = 3.1 \text{ k}\Omega$$

(b)

For M₂:
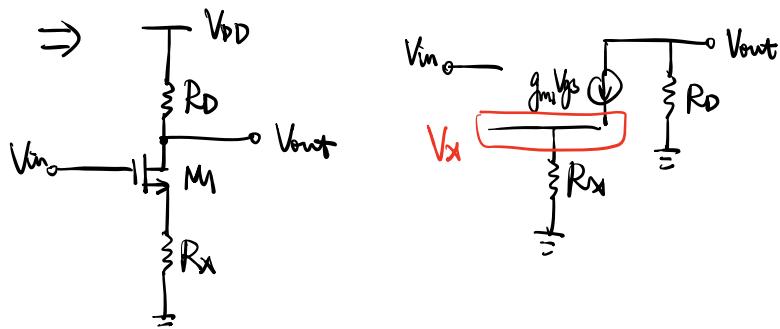
$$\left\{ \begin{array}{l} V_{gs} = -V_x \\ i_x = -g_{m2} V_{gs} \end{array} \right. \Rightarrow R_x = \frac{V_x}{i_x} = \frac{1}{g_{m2}}$$



$$\left\{ \begin{array}{l} V_{out} = -g_{m1} V_{gs} R_D \quad (1) \\ V_x = g_{m1} V_{gs} R_x \quad (2) \\ V_{gs} = V_{in} - V_x \quad (3) \end{array} \right.$$

$$(2), (3): V_x = \frac{g_{m1} R_x}{g_{m1} R_x + 1} V_{in} \quad (4)$$

$$(1), (3), (4): A_V = \frac{V_{out}}{V_{in}} = -g_{m1} R_D \left(1 - \frac{g_{m1} R_x}{g_{m1} R_x + 1} \right) = -\frac{g_{m1} g_{m2} R_D}{g_{m1} + g_{m2}}$$

$$\therefore A_V = -\frac{g_{m1} g_{m2} R_D}{g_{m1} + g_{m2}}$$