

---

## VE311 Electronic Circuit Homework 6

Due: December 17th (no late submission)


---


*Note:*

- 1) Please use A4 size paper or page.
- 2) Please clearly state out your final result for each question.
- 3) Please attach the screenshot of Pspice simulation result if necessary.
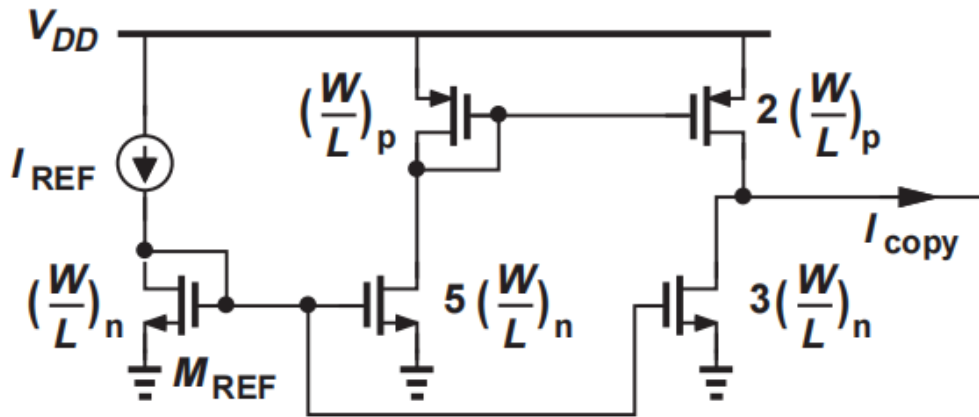
### Question 1. Current Mirror 1

[30pts] Calculate  $I_{copy}$  in the circuit shown below. Assume all the transistors operate in saturation.



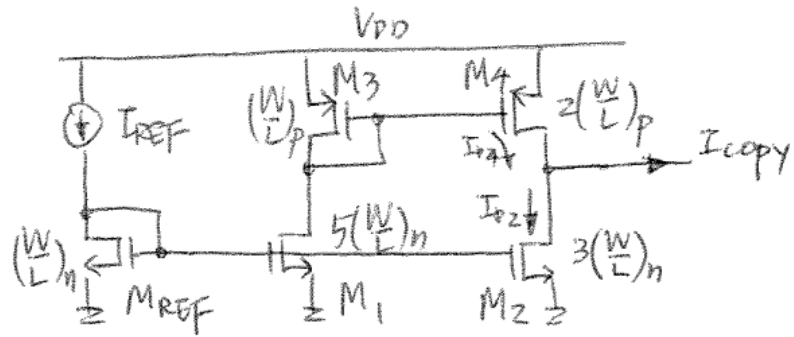

$$V_{GS, REF} = V_{GS, 1} \therefore I_{D, 1} = 5 I_{REF}$$

$$V_{GS, 3} = V_{GS, 4} \therefore I_{D, 4} = 2 I_{D, 3} = 2 I_{D, 1} = 10 I_{REF}$$


$$V_{GS, REF} = V_{GS, 2} \therefore I_{D, 2} = 3 I_{REF}$$


$$\therefore I_{copy} = I_{D, 4} - I_{D, 2} = 7 I_{REF}.$$

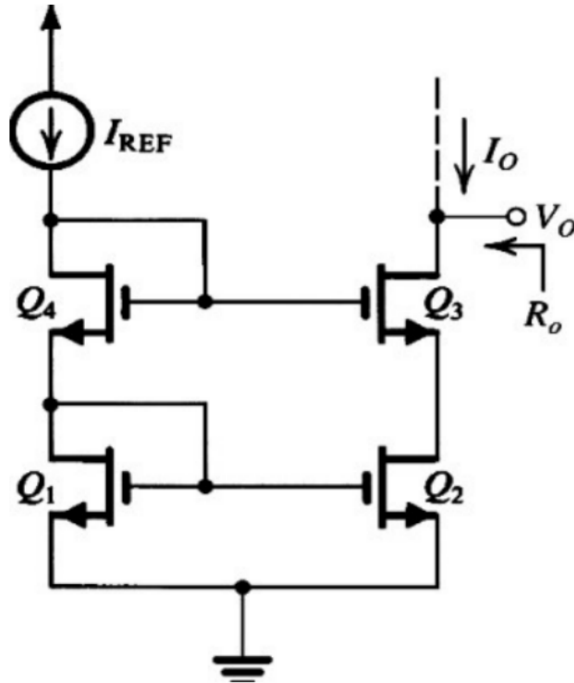**Question 2. Current Mirror 2**

[70pts] In a particular cascaded current mirror shown below, assume all transistors have  $V_{TH} = 0.7V$ ,  $\mu_n C_{ox} = 160\mu A/V^2$ ,  $L = 1\mu m$ . For the widths,  $W_1 = W_4 = 4\mu m$  and  $W_2 = W_3 = 40\mu m$ . The reference current  $I_{REF} = 20\mu A$ . No body effect.

- Assume  $\lambda = 0$ , what is the output current result  $I_O$  and the voltages at the gates of  $Q_2$  and  $Q_3$ ?
- Assume  $\lambda = 0$ , what is the lowest voltage at the output for which current-source operation is possible?
- Assume  $\lambda = 0.1$  and the  $I_O$  keeps with the value that obtained from (a) and (b), what are the values of  $g_m$  and  $r_o$  of  $Q_2$  and  $Q_3$ ? What is the output resistance of the mirror?



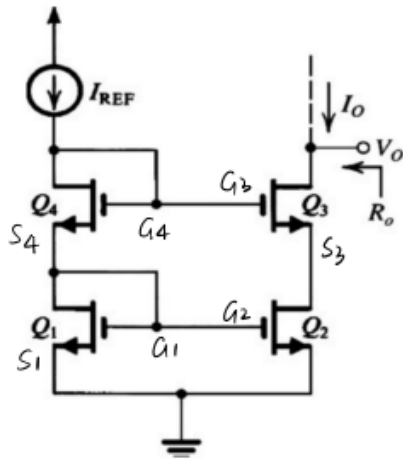

$$(a). I_{REF} = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L} (V_{GS1} - V_{TH})^2 = 20 \mu A.$$

$$\Rightarrow V_{G1} = 0.95 V$$

$$\therefore V_{G2} = V_{G1} = 0.95 V$$

$$I_0 = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L} (V_{GS2} - V_{TH})^2 = 200 \mu A$$

$$\therefore I_{REF} = \frac{1}{2} \mu_n C_{ox} \frac{W_4}{L} (V_{GS4} - V_{TH})^2 = 20 \mu A$$

$$\Rightarrow V_{GS4} = 0.95 V$$

$$\therefore V_{S4} = V_{G1} = 0.95 V \quad \therefore V_{G4} = 1.9 V$$

$$\therefore V_{G3} = V_{G4} = 1.9 V$$


$$(b). V_{DS3} \geq V_{GS4} - V_{TH}$$

$$V_0 - V_{S3} \geq V_{G3} - V_{S3} - V_{TH}$$

$$\Rightarrow V_0 \geq V_{G3} - V_{TH} = 1.2 V$$

$$(c). g_{m2} = \frac{2I_0}{V_{GS2} - V_{TH}} = 1.6 \times 10^{-3} A/V = g_{m3}$$
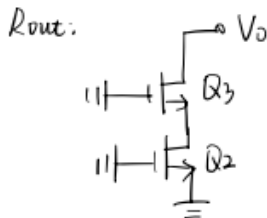
$$r_{o2} = \frac{1}{I_0 \cdot \lambda} = 5 \times 10^4 \Omega = r_{o3}$$



Cascode circuit without  $R_D$  and  $g_{mb}$ ,

$$\text{Original formular: } R_{out} = [r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o1}r_{o2}] \parallel R_D$$

Ignore  $R_D$  and  $g_{mb}$ , we get:

$$R_{out} = r_{o2} + r_{o3} + g_{m3}r_{o2}r_{o3} = 4.1 \times 10^6 \Omega$$

$$\text{If } Q_1, Q_4 \text{'s } \lambda = 0.1, I_{REF} = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L} (V_{GS1} - V_{TH})^2 (1 + \lambda V_{DS1})$$

$$\Rightarrow V_{GS1} = V_{DS1} = V_{G1} = V_{G2} = 0.94 V$$

$$\therefore g_{m2} = g_{m3} = \frac{2I_0}{V_{GS2} - V_{TH}} = 1.67 \times 10^{-3} A/V$$

$$\therefore r_{o2} = \frac{1}{I_0 \lambda} = 5 \times 10^4 \Omega = r_{o3}$$

$$R_{out} = r_{o2} + r_{o3} + g_{m3}r_{o2}r_{o3} = 4.28 \times 10^6 \Omega$$