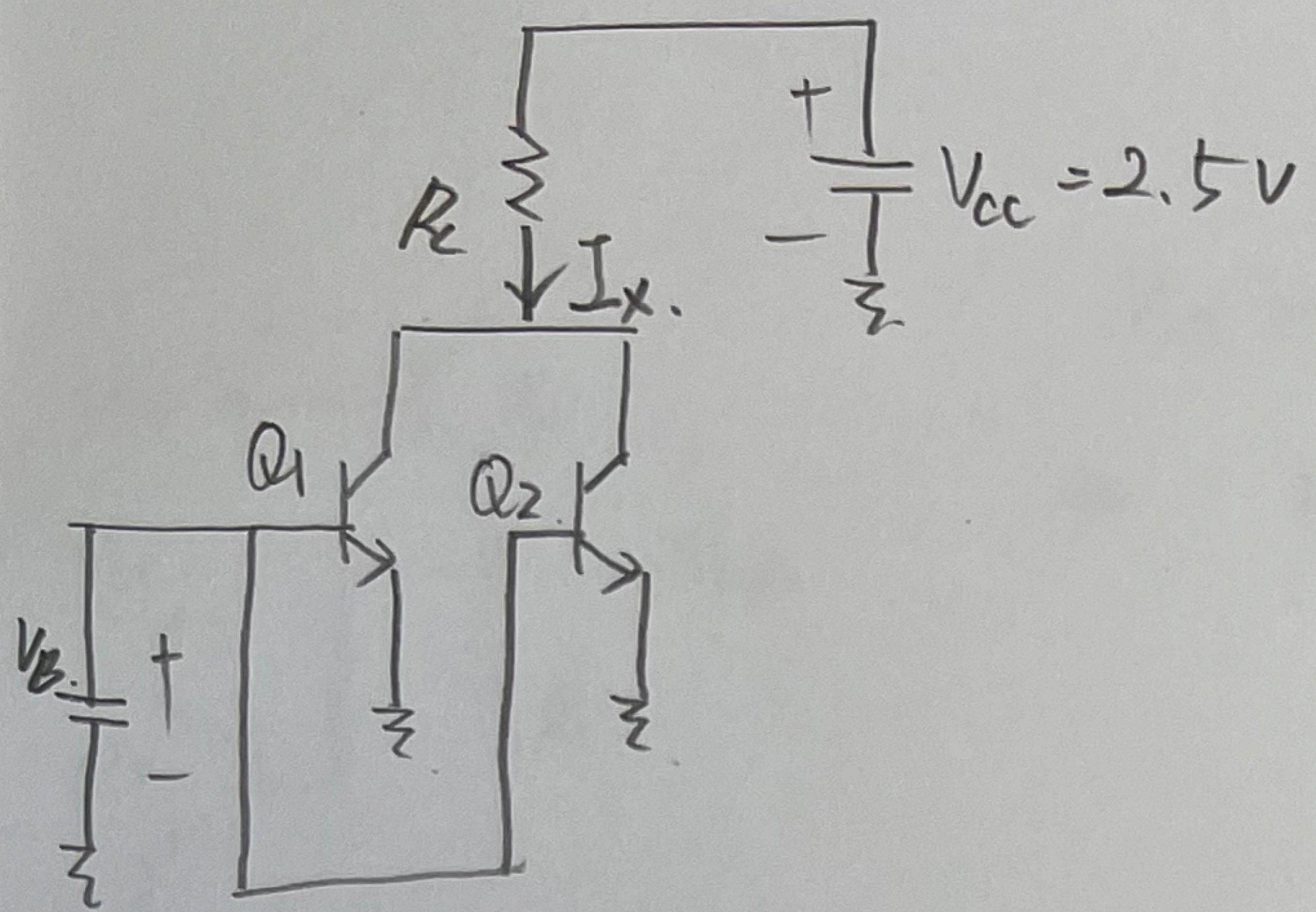


QWZ1



$$I_{S1} = 2I_{S2} = 5 \times 10^{-16} A$$

$$I_x = 1.2 \text{ mA}$$

$$V_B = ?$$

$$I_{C1} = I_{S1} \left[\exp \left(\frac{V_B}{V_T} \right) - 1 \right]$$

$$I_{C2} = \frac{1}{2} I_{S2} \left[\exp \left(\frac{V_B}{V_T} \right) - 1 \right]$$

$$I_x = \frac{3}{2} I_{S1} \left[\exp \left(\frac{V_B}{V_T} \right) - 1 \right] = 1.2 \text{ mA}$$

$$5 \times 10^{-16} \quad \text{use } V_T = 0.026$$

$$\text{then } \underbrace{V_B = 0.731 \text{ V}}$$


Voltage drop at $R_C = R_C \times I_x$

$$V_{CE} = 2.5 - R_C I_x \geq V_{BE}$$

$$\Rightarrow 2.5 - R_C \times 1.2 \times 10^{-3} = 0.731 \quad \text{edge of active mode.}$$

$$R_C = 1474.17 \Omega$$

Ques 1

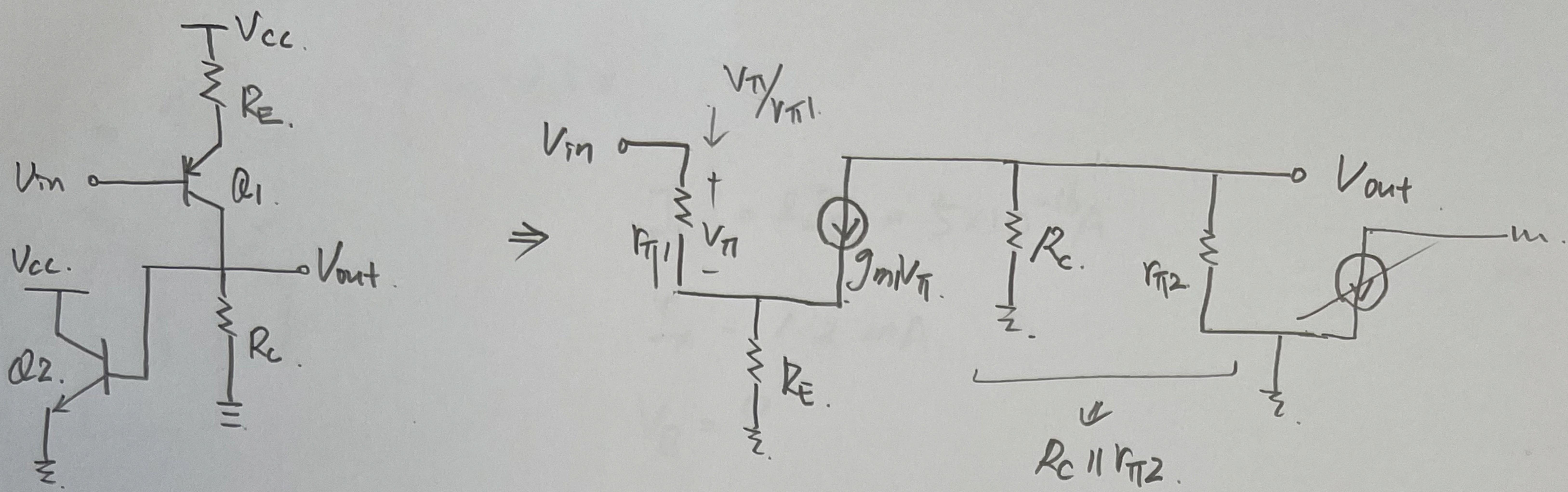

$$V_{out} = -g_m V_\pi (R_c \parallel r_{\pi 2})$$

$$-V_{in} + V_\pi + \left(R_E \left(V_\pi / r_\pi + g_m V_\pi \right) \right) = 0$$

$$V_{in} = \underline{\underline{V_\pi}} \left(1 + \frac{R_E}{r_{\pi 1}} + g_m R_E \right)$$

$$V_{out} = -g_m \cdot \frac{V_{in}}{1 + \frac{R_E}{r_\pi} + g_m R_E} (R_c \parallel r_{\pi 2})$$

$$A_v = -g_m \cdot \frac{R_c \parallel r_{\pi 2}}{1 + \frac{R_E}{r_{\pi 1}} + g_m R_E} \quad \text{or} \quad -g_m \cdot \frac{R_c \parallel r_{\pi 2}}{1 + g_m R_E}$$

or seen from the small-signal model

the circuit is C-E stage with emitter degeneration.

$$A_v = - \frac{g_m R_c}{1 + g_m R_E} \Rightarrow - \frac{g_m (R_c \parallel r_{\pi 2})}{1 + g_m R_E}$$